

Device Physics

413

$$\phi = - \int_0^L \vec{E} \cdot d\vec{l}$$

$$F_e = -qE$$

$$\langle v \rangle = \mu_n \vec{E} \quad \text{where } \mu_n = \frac{-qT}{m^*} \quad [\text{cm}^2/\text{Vs}]$$

$$J = n \mu_n \vec{E} q = \sigma \vec{E}$$

In H & other atoms

$$E_{\text{tot}} = \frac{-13.6 \text{ (eV)}}{n^2} = -\frac{p^2}{2m}$$

where,

$$p = \frac{m}{2E} \cdot \frac{q^2}{nh}$$

Depends on E_g & carrier conc. in bands.

$\phi \rightarrow$ potential

$E \rightarrow$ Electric field.

$\nabla \rightarrow$ Potential difference

$F_e \rightarrow$ Force on an e.

$\langle v \rangle \rightarrow$ avg. velocity in one direction

$\mu_n \rightarrow$ mobility.

$T \rightarrow$ avg time b/w collisions.

$m^* \rightarrow$ effective mass

$J = \frac{I}{A}$ current density.

$\sigma =$ Conductivity

$$= \frac{1}{\rho}$$

$E_{\text{tot}} =$ Energy of e in nth level.

$$E_{gSi} = 1.12 \text{ eV.}$$

$$h = \text{Planck's const} = 6.62 \times 10^{-34} \text{ Js}$$

$\epsilon =$ permittivity.

$n =$ energy level.

$E_F =$ Fermi level.

$E =$ Energy level

$n_p =$ no. of e/h+ in CB/VB.

$$k = 1.38 \times 10^{-23} \text{ m}^2 \text{ kg s}^{-2} \text{ K}^{-1}$$

Carrier distribution (Fermi Dirac Distribution)

$$f(E) = \frac{1}{1 + e^{\frac{E-E_F}{KT}}}$$

Prob. of E_F to be occupied = 50%.

$\xrightarrow{E_F}$ Prob. of finding an electron at room temp. = 50%. (Semi conductors)

$\rightarrow$ All levels below E_F are filled with e's at 0K & all levels above are empty. (metals)

when $E-E_F \gg 3KT$

$$f(E) \approx e^{\frac{E_F-E}{KT}} \quad (\text{Boltzmann distribution})$$

$$n = N_c e^{\frac{E_F-E_c}{KT}}$$

$$p = N_v e^{\frac{E_v-E_F}{KT}}$$

Intrinsic Silicon

$$E_F = \frac{E_C + E_V}{2}$$

$$E_F = E_i \quad \times \quad n_i = p_i$$

$$n_i p_i = n_i^2$$

$$N_A^- + n^- = N_D^+ + p^+ \quad *$$

n_i is used as a reference point.

Boron $[-ve \text{ ions}] N_A = \text{conc. of acceptors}$

Phos. $[+ve \text{ ions}] N_D = \text{conc. of donors}$

$n = \text{conc. of electrons}$

$p = \text{conc. of holes}$

units (cm^{-3}) .

Motion of Carriers

Drift:- Current due to electric field. (minority)

Note:- (q does not have sign)

$$\begin{aligned} J_n &= (n q \mu_n) \vec{E} = \nabla_n \vec{E} \\ J_p &= (p q \mu_p) \vec{E} = \nabla_p \vec{E} \end{aligned} \quad \left. \vphantom{\begin{aligned} J_n \\ J_p \end{aligned}} \right\} \vec{J} = \vec{J}_n + \vec{J}_p$$

$$[\mu_p < \mu_n]$$

Diffusion:- Current due to carrier conc. gradient $\times$ random motion (majority)

$$J = -q D \frac{\partial p}{\partial x}$$

$$\frac{D}{\mu} = \frac{kT}{q}$$

p = charge density

Note:- q is $-ve$ for e^- & $+ve$ for h^+

Energy = $q(\text{potential})$

Field = $\nabla(\text{potential})$

PN junction

e^- (minority)

e^- diffusion.

e^- (majority)

e^- drift

$q\psi_0$ = Built in potential



Forward bias (+V_D)

$$I_D(V_D) = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right)$$

Reverse bias (-V_D)

$$I_D(V_D) = I_S \left(e^{-\frac{V_D}{V_T}} - 1 \right) \approx -I_S$$

$$V_T = \frac{KT}{q} \text{ thermal Voltage}$$

$$I_S = \text{const.}$$

Junction Capacitance $C_j = \frac{\epsilon_s}{x_n + x_p}$

$$\left\{ \begin{aligned} \phi_p &= \frac{q N_A x_p^2}{2 \epsilon_s} \\ \phi_n &= \frac{q N_D x_n^2}{2 \epsilon_s} \end{aligned} \right\} \left\{ \begin{aligned} &\text{From} \\ &\text{①, ② \& ③} \end{aligned} \right\} \text{④}$$

$$\vec{E} = -\frac{d\phi}{dx} \Rightarrow \phi = -\int \vec{E} \cdot d\vec{x} \text{ ③}$$

$$\vec{E} = -\frac{1}{\epsilon_s} \int_{x_1}^{x_2} \rho(x) dx \text{ ②}$$

doping conc. = $q N_D, -q N_A$
↳ ①

Drift = Diffusion $\Rightarrow \left\{ \begin{aligned} \phi_p &= -\frac{KT}{q} \ln \frac{N_A}{n_i} \\ \phi_n &= \frac{KT}{q} \ln \frac{N_D}{n_i} \end{aligned} \right\} \text{⑤}$

Barrier pot.
 $\phi_0 = |\phi_p| + |\phi_n|$

* $x_n N_D = x_p N_A$.
(Total charge on both sides)

④ & ⑤

$$\therefore \phi_0 = \frac{KT}{q} \ln \frac{N_D N_A}{n_i^2} = \frac{1}{2} q \frac{N_A}{\epsilon_s} x_p^2 \left(1 + \frac{N_A}{N_D} \right)$$

Solving

$$x_p = \sqrt{\frac{2 \epsilon_s}{q N_A} \cdot \frac{N_D}{N_A + N_D} \cdot \phi_0}$$

$$x_n = \sqrt{\frac{2 \epsilon_s}{q N_D} \cdot \frac{N_A}{N_A + N_D} \cdot \phi_0}$$

Depletion width = $x_p + x_n$.

$$x = \sqrt{\frac{2 \epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) \phi_0}$$

$$C_j = \left[\frac{q \epsilon_s}{2 \left(\frac{1}{N_A} + \frac{1}{N_D} \right) \phi_0} \right]^{\frac{1}{2}} = \frac{C_{j0}}{\sqrt{1 - \frac{V_D}{\phi_0}}} \quad C_{j0} = C_j \text{ when } V_D = 0$$

Replace with
in V_D when biased.

MOS CAP
For p type


Accumulation; Weak/Strong inversion
[$V_g > 0$] [$V_g < 0$]

→ This is where we operate & channel forms.

It has n bulk.

$$E_{Fm} - E_{Fs} = -qV_g$$

Strong inversion

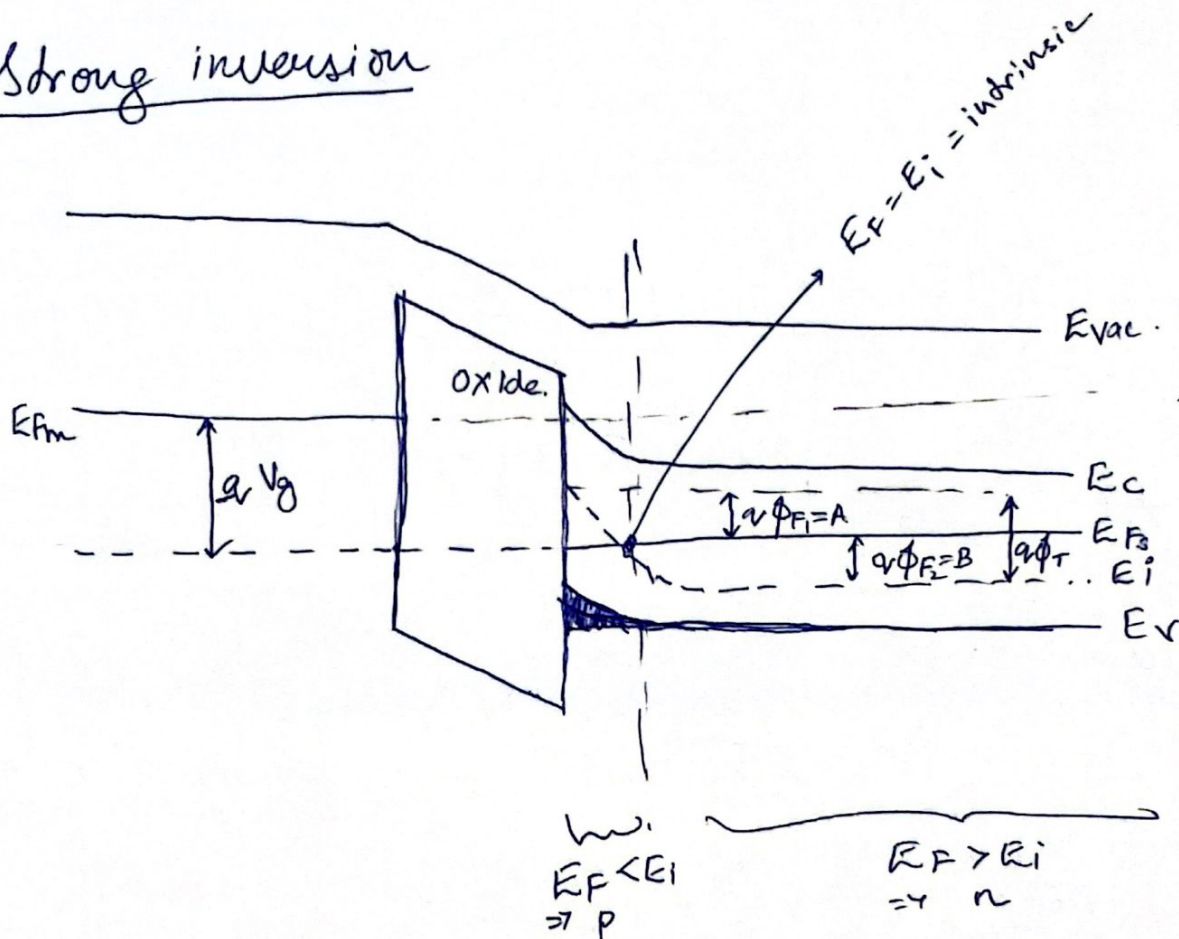

Strong inversion. ($V_g = V_{th}$)

A → potential of 'p' at oxide surface.

B → potential of 'n' at bulk of substrate

A = B

$$\Rightarrow q\phi_{Fi} = q\phi_{Fs} = q\phi_F$$

$$\therefore \phi_T = 2\phi_F = \frac{2}{q}(E_F - E_i)$$

Let potential drop across oxide = ϕ_{ox}

$$\therefore V_g = \Delta\phi_{ox} + \phi_T$$


Change in Fermi level of SC is higher than change in E_i , E_c & E_v .

Change in $F_L \Rightarrow V_g$

Change in E_i , E_c & $E_v \Rightarrow \phi_T$

$$\phi_T = \frac{2KT}{q} \ln \frac{N_D}{n_i}$$

$$V_{th} = \phi_T + \Delta \phi_{ox}$$

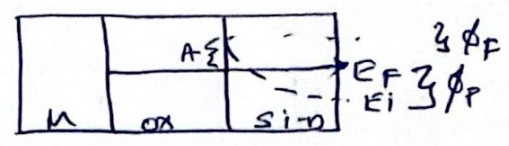

$$x_d = \sqrt{\frac{2 \epsilon_{si} \phi_T}{q N_D}}$$

width of depletion region in Si.

$$|E_{si}(x=0)| = \sqrt{\frac{2 q N_D \phi_T}{\epsilon_{si}}}$$

$$E_{ox} = \frac{\epsilon_{si}}{\epsilon_{ox}} \sqrt{\frac{2 q N_D \phi_T}{\epsilon_{si}}}$$

$\downarrow$
 $\frac{\Delta \phi_{ox}}{t_{ox}}$

$$V_{th} = \phi_T + \Delta \phi_{ox}$$

$$V_{th} = 2\phi_F + \frac{\epsilon_{si}}{\epsilon_{ox}} t_{ox} \sqrt{\frac{2 q N_D \phi_T}{\epsilon_{si}}}$$

where, $\phi_T = 2\phi_F$

$$\phi_F = \frac{kT}{q} \ln \frac{N_D}{N_i}$$

$$V_{th} = 2\phi_F + \gamma \sqrt{2\phi_F}$$

where,

$$\gamma = \frac{\sqrt{2 q \epsilon_{si} N_D}}{C_{ox}}$$

In reality;

$$V_{th} = V_{FB} + 2\phi_F + \gamma \sqrt{2\phi_F} \quad \text{or}$$

$$V_{th} = V_{th0} + \gamma \sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F}$$

$V_{FB} \rightarrow$ Flatband Voltage
if the band is not flat $\rightarrow$ if carriers inside oxide

$$V_{FB} = \phi_{ms} - \frac{Q_{ss}}{C_{ox}} - \frac{Q_{ox}}{C_{ox}}$$


Changes ~~in the~~ surface & in oxide

ph type mos	n bulk	↑ve. V_{GS} accumulations.	-ve. V_{GS} inversion
n type mos	p bulk	↑ve. V_{GS} inversion.	-ve. V_{GS} accumulation

In MOSFET strong inversion is much faster

- 2 n^+ sources

- V_{SB}

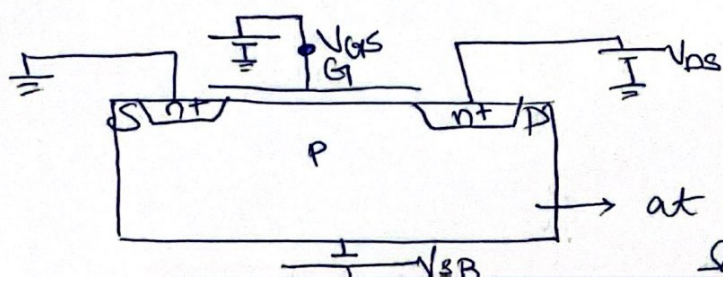

at negative for easy strong inversion.

When $V_{SB} \neq 0$

$$V_{th} = V_{FB} + 2\phi_F + \gamma \sqrt{2\phi_F + V_{SB}}$$

$\Rightarrow V_{th}$ increases.

Current in MOSFET

$$V_{GS} > V_{th}$$

V_{DS} is small $\approx$ true.

$$\Rightarrow I_D = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) V_{DS} \text{ acts as resistor.}$$

V_{DS} is large.

$$V_{DS} \leq V_{GS} - V_{th}$$

Triode

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

still not a current source

V_{DS} is even larger $\Rightarrow$ pinch off.

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [V_{GS} - V_{th}]^2$$

$V_{DS} = V_{GS} - V_{th}$
 $L = L'$
 not ideal since
 L' depends on V_{DS} .
 (CLM)

$$\text{let } \lambda = \frac{1}{V_A} = \frac{\partial I_D / \partial V_{DS}}{I_D} = \frac{1}{L'} \cdot \frac{\partial x_d}{\partial V_{DS}}$$

$$V_{DS} \geq V_{GS} - V_{th}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [V_{GS} - V_{th}]^2 [1 + \lambda V_{DS}] \rightarrow \text{CLM}$$


for ideal transistor: $\lambda \downarrow \Rightarrow$ $L \uparrow$ or Doping $\uparrow$

Both have issues.

CLM Channel length modulation.

$V_{DS} \uparrow \Rightarrow x_d \uparrow \Rightarrow L' \downarrow \Rightarrow$ not ideal.

Sub threshold effect

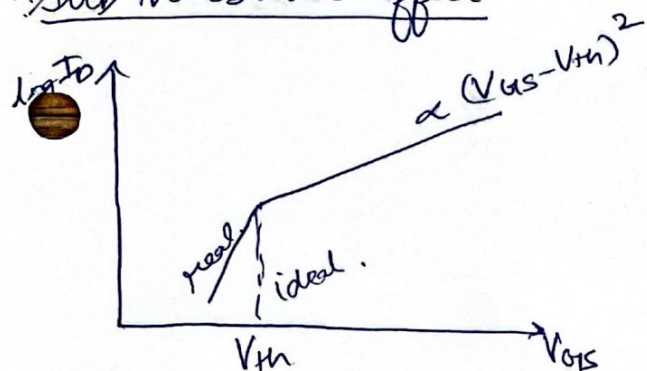

$$I_D \propto \frac{W}{L} e^{\frac{V_{GS}}{nV_T}}$$


$$g_m = \frac{I_D}{nV_T}$$

We can use it by lowering V_{GS} & increasing $\frac{W}{L} \Rightarrow$ high gain but more parasitic capacitances.

Velocity saturation [Short channel devices]

Drift velocity saturates as $E \uparrow$

$$v_d = \mu E \text{ when } E < E_c$$

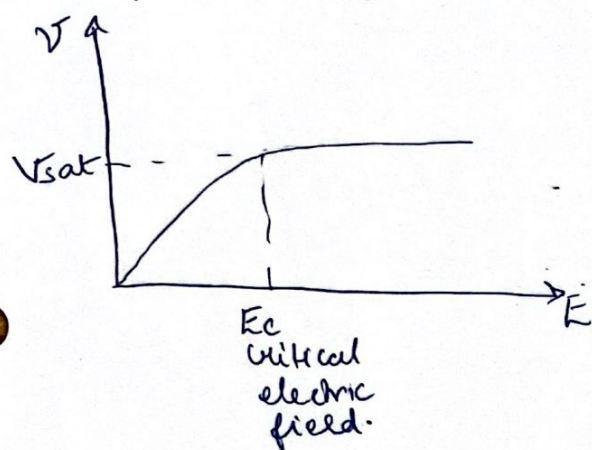

Use $\mu = \frac{\mu_0}{1 + \frac{E}{E_c}}$ to model this effect.

$$I_D = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} \cdot \frac{(V_{GS} - V_{th})^2}{1 + \frac{V_{GS} - V_{th}}{E_c \cdot L}}$$

Assuming $\frac{V_{GS} - V_{th}}{E_c \cdot L} \gg 1 \Rightarrow I_D = \frac{\mu_n C_{ox}}{2} \cdot E_c W (V_{GS} - V_{th})$

$$\therefore I_D \propto (V_{GS} - V_{th}) \Rightarrow g_m = \frac{\partial I_D}{\partial V_{GS}} = \text{const.}$$

General

$$I_D \propto (V_{GS} - V_{th})^m$$

$1 \leq m \leq 2$
 $\swarrow$ small channel
 $\searrow$ large channel.

Effects of Small dimensions

- ① Velocity saturation.
- ② lower V_{th} because s.d depletion regions are significant.
- ③ Hot electron effect. (Thin silicon channel) ④ DIBL. (lower r_o)

Voltage controlled current source Transconductance



$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})$$

$g_m \propto \sqrt{I_D}$


ignore λ .

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$$

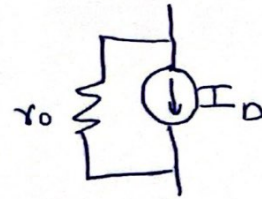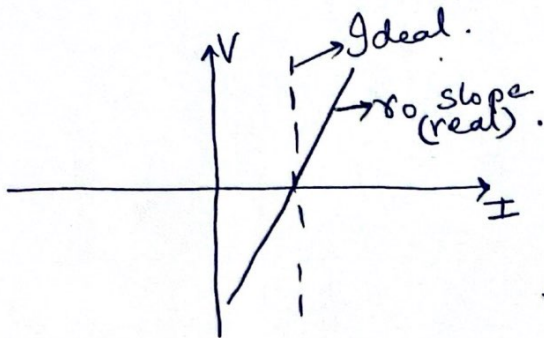we can model this nonlinearity as a resistor. r_o



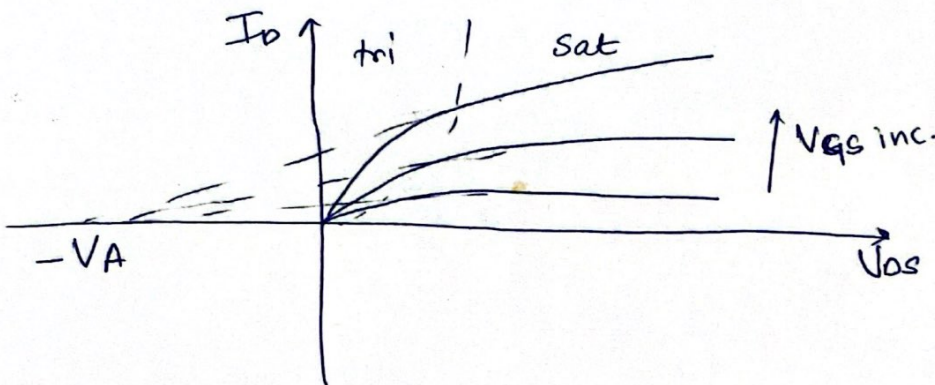
$$r_o = \frac{\partial I_D}{\partial V_{DS}} = \frac{1}{\lambda I_D} = \frac{V_A}{I_D} \rightarrow \text{Early voltage.}$$



$$\lambda = \frac{1}{L'} \left[\frac{d\lambda}{dV_{DS}} \right]$$

Body effect

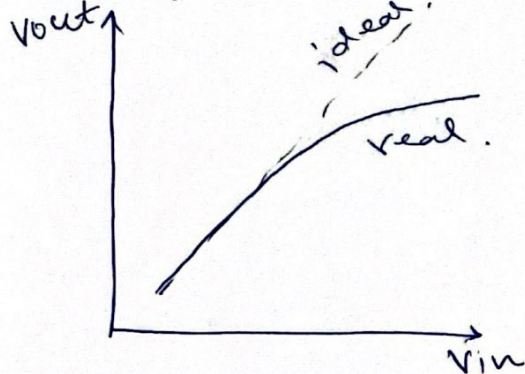

$$V_{in} \uparrow \Rightarrow V_{out} \uparrow \Rightarrow V_S \uparrow \Rightarrow V_{SB} \uparrow \Rightarrow V_{th} \uparrow \Rightarrow I_D \downarrow$$

I_D is affected by channel length modulation & body effect.

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}}$$

$$g_{mb} = g_m \left(-\frac{\partial V_{th}}{\partial V_{BS}} \right)$$

To fix it

→ Connect S & B



→ $\gamma \downarrow \Rightarrow N_A \downarrow$

$$g_{mb} = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}} \cdot g_m = \chi g_m$$

$\chi = \sqrt{2\phi_F + V_{SB}}$

Small signal model

9

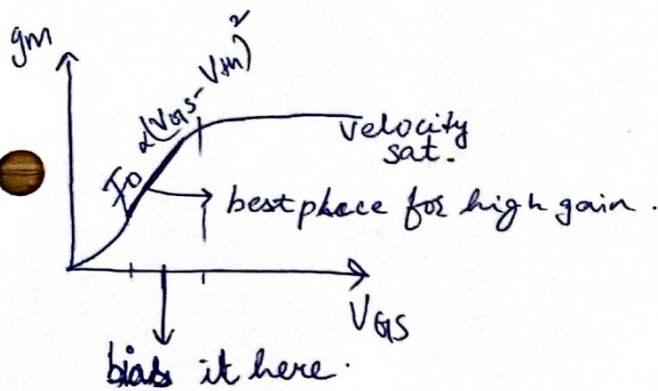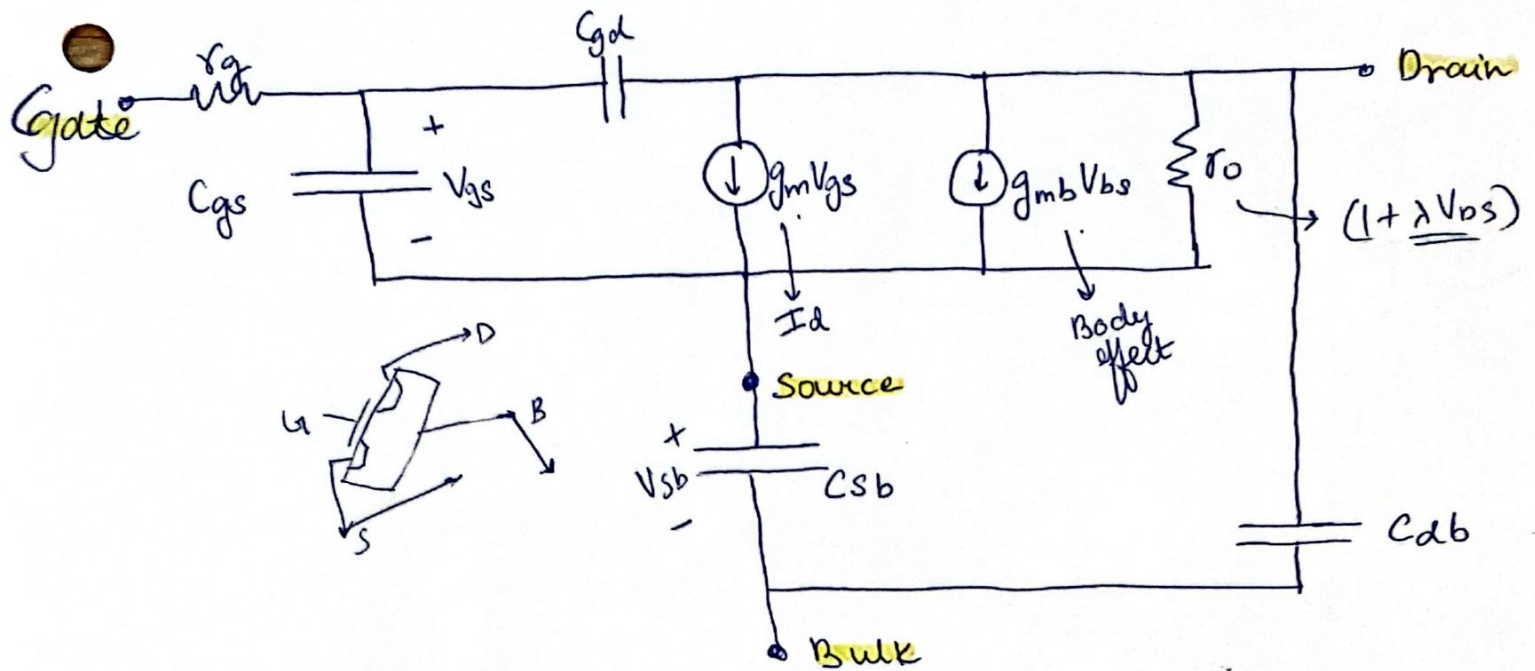


Cut off frequency
when current gain = 1

$$f_T = \frac{1}{2\pi} \frac{g_m}{C_{gs} + C_{gd}}$$

$f_T \propto \frac{V_{sat}}{L} \rightarrow$ limiting factor of f_T is architecture.

Amplifier Design

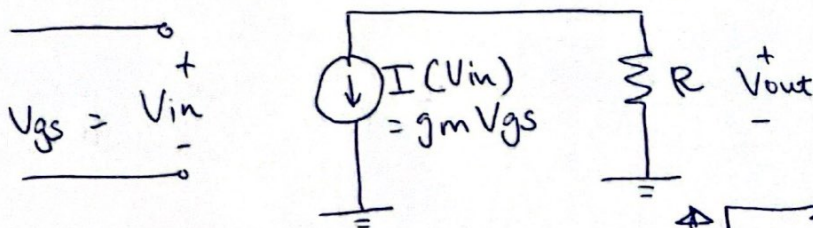


$$V_{out} = R I(V_{in})$$

$$V_{out} = R \cdot g_m \cdot V_{in}$$

gain

$$A_v = \frac{V_{out}}{V_{in}} = g_m \cdot R$$


Common Source

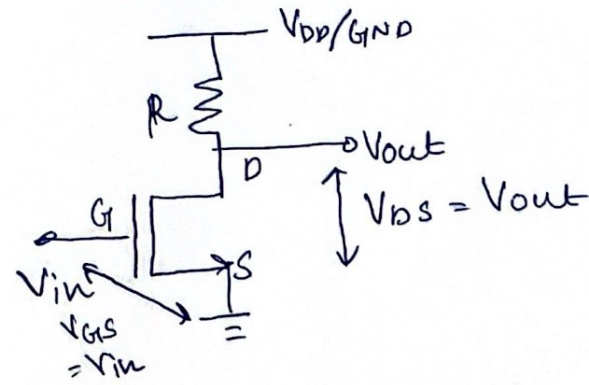

Large signal (Always equate currents)

$$V_{out} = V_{DD} - I_D R_D$$
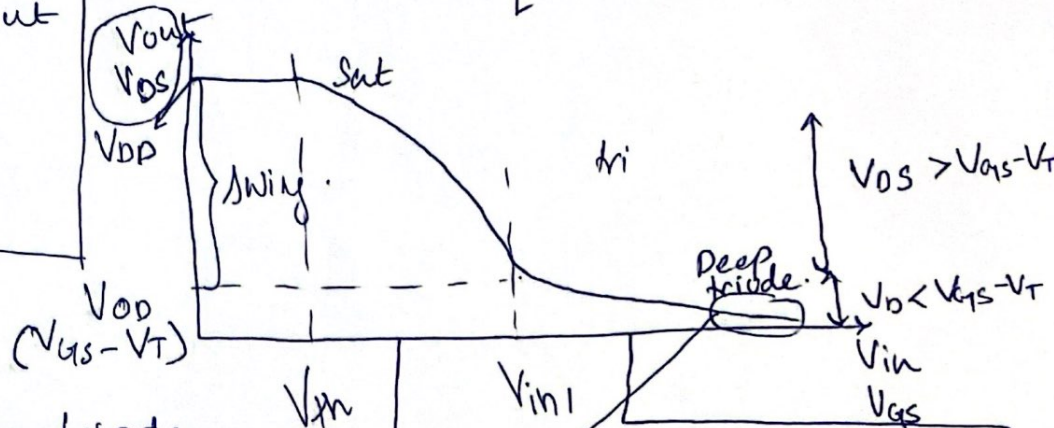
$$= V_{DD} - R_D \left[\frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} \cdot (V_{in} - V_{th})^2 \right]$$




Gain in sat

$$A_v = \frac{\partial V_{out}}{\partial V_{in}}$$

$$A_v = -g_m R_D$$

Deep triode
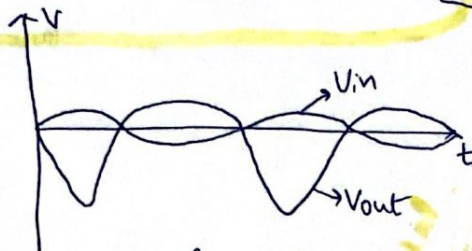
$$V_{out} = \frac{V_{DD}}{1 + \mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{th})}$$



nonlinear gain.

$$V_{in} \downarrow \Rightarrow I_D \downarrow \Rightarrow g_m \downarrow \therefore (V_{GS} \downarrow)$$

$$I_D = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} [V_{GS} - V_{th}]^2$$

$$I_D = \mu_n C_{ox} \frac{W}{L} [(V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2}]$$

$$I_D = \mu_n C_{ox} \frac{W}{L} [(V_{GS} - V_{th}) V_{DS}]$$

resist

Tradeoffs $\rightarrow R_D I_D (\text{const})$

Const Swing:- $I_D \uparrow \Rightarrow \text{gain} \downarrow \Rightarrow R_D \downarrow \Rightarrow g_m \uparrow \Rightarrow g_m R_D \downarrow$

(const swing)

① Tradeoff b/w const. swing $\times$ gain $\times$ size

overcome.

Size effects:-

$$\frac{W}{L} \uparrow \Rightarrow I_D \uparrow \Rightarrow g_m \uparrow \Rightarrow R_D \downarrow \Rightarrow \text{Constant gain. but bulky & slow.}$$

(const swing)

Swing (const)


VS

Gain

VS

$\frac{W}{L}$

Small signal model:-


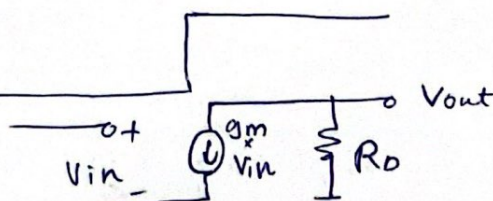


Output r_o


$$r_o = \frac{1}{\lambda I_D}$$

$$A_v = -g_m \frac{R_D r_o}{R_D + r_o}$$

$\Rightarrow r_o$ & R_D are in parallel.

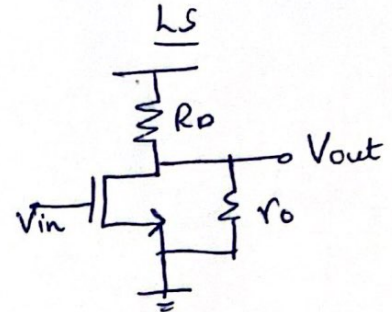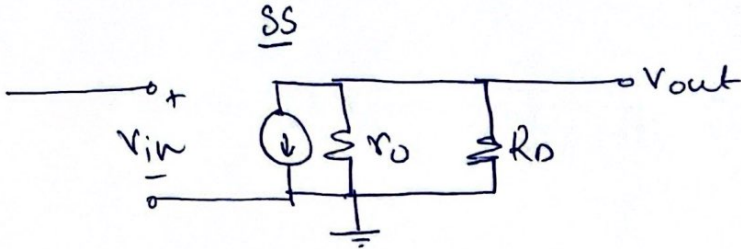

Diode connected transistor

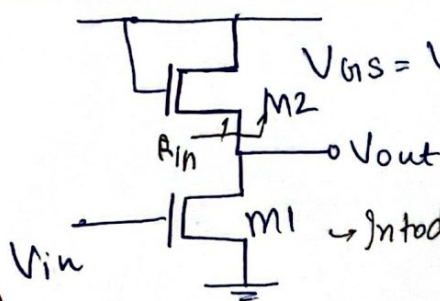


$V_{GS} = V_{DS} \Rightarrow V_{DS} > V_{GS} - V_{th} \Rightarrow$ only sat. or off

Intoday's technology

$$A_v = -g_{m1} \left[\frac{1}{g_{m2}} \parallel r_{o1} \parallel r_{o2} \right]$$

$$\chi = \frac{\sqrt{2\mu C_{ox} N_A} \phi_p}{2(2|\phi_p| + V_{SD})^2}$$

M2 Find R_{in}

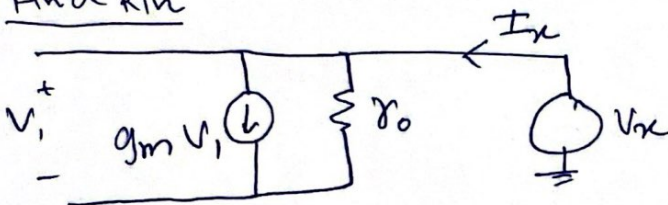


$$R_{in} = \frac{v_x}{i_x} \quad (v_1 = v_x)$$

$$i_x = g_m v_1 + \frac{v_x}{r_o}$$

$$R_{in} = \frac{1}{g_m + \frac{1}{r_o}} = \left(\frac{1}{g_m} \parallel r_o \right)$$

$$R_{in} \approx \frac{1}{g_m} \quad r_o \gg \frac{1}{g_m}$$

Body effect (Small signal)

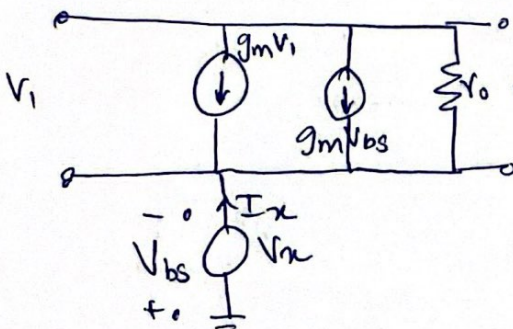

$$v_1 = v_{bs} \begin{cases} v_{bs} = -v_x \\ v_1 = -v_x \end{cases}$$

$$R_{out} = r_{o1} \parallel R_{in}$$

$$R_{in} \approx \frac{1}{g_m + g_{mb}}$$


$$R_{in} = \frac{1}{g_m + g_{mb} + \frac{1}{r_o}}$$

lower gain
but
pretty
wrt temp $\rightarrow$ constant

$$A_v = - \sqrt{\left(\frac{W}{L} \right)_1 / \left(\frac{W}{L} \right)_2} \cdot \frac{1}{1 + \chi}$$

$\frac{g_{mb2}}{g_{m2}} \rightarrow \frac{\partial V_{th2}}{\partial V_{out}}$

Using PMOS to eliminate Body effect

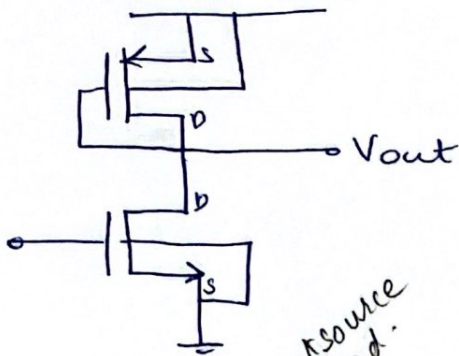


$$A_v = -g_{m1} \cdot \frac{1}{g_{m2}}$$

$$A_v = \sqrt{\frac{\mu_n}{\mu_p} \left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2}$$

not so more linear
but temp change issue

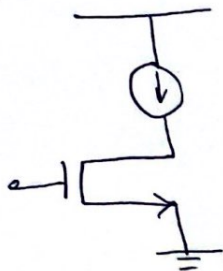
Active load is little different
Active load → current source load.




- current source as load.

$$A_v = -g_m r_o$$

$$A_v = \frac{2 V_A}{V_{DD}}$$

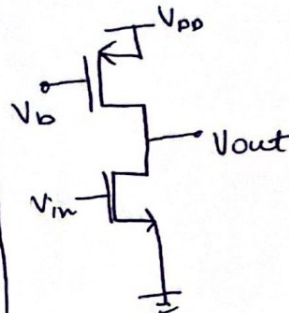


$$A_v = -g_m (r_{o1} || r_{o2})$$

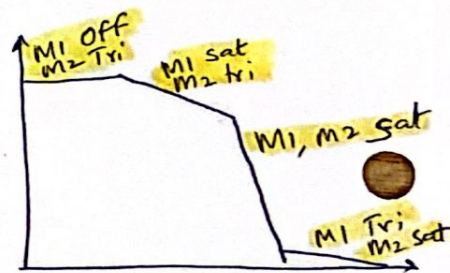

For large swing $\Rightarrow V_{b1} \uparrow$
For high gain $\Rightarrow W \uparrow$ but slow

Source degeneration

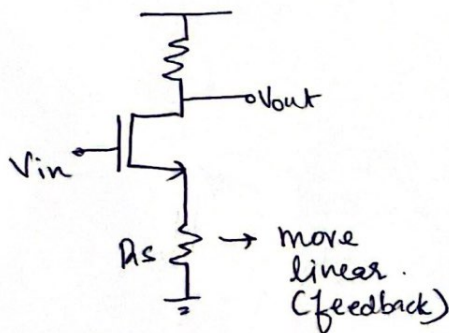

$$A_v = \frac{g_m r_o}{1 + [1 + (g_m + g_{mb}) R_s] r_o}$$

$$A_v = \frac{-g_m R_o}{1 + g_m R_o} = \frac{-g_m r_o R_o}{R_o + R_s + r_{o1} (g_m + g_{mb}) R_s r_o}$$

$$G_m = \frac{g_m}{1 + g_m R_s}$$

Trading gain for linearity.

$$= \frac{g_m}{1 + (g_m + g_{mb} + \frac{1}{r_o}) R_s}$$

$\rightarrow R_s$ gives a negative feedback proportional to R_s .

$$\Delta V_{in} = \Delta V_{GS} + \Delta V_{RS} \rightarrow R_s g_m \Delta V_{GS}$$

$$R_{out} = r_o [1 + (g_m + g_{mb}) R_s]$$

boosts R_s by $g_m r_o$

$\rightarrow$ to find R_{out} we ground the gate input.

Story of the transistor

13

→ Amplifier design

Common source

$$A_v = -g_m R_D$$

$$A_v = -g_m (r_{o1} \parallel R_D)$$

Non-linear (g_m varies with V_{in})

Not very high gain.

Swing vs. speed vs. Gain
($\frac{W}{L}$)

Diode connected MOSFET

$$A_v = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \cdot \frac{1}{1+\chi}$$

→ lower gain

→ More linear

PMOS Diode connected MOSFET

$$A_v = -\sqrt{\frac{\mu_n (W/L)_1}{\mu_p (W/L)_2}}$$

Even More linear

→ Depends on process & temp

... So far gain has been quite low.
Need large r_o but small R_D (A_v)

Active load MOSFET (Ideal)

$$A_v = -g_m r_o = \frac{2 V_A}{V_{DD}}$$

Active load MOSFET (Nonideal) - [PMOS with V_b]

$$A_v = -g_{m1} (r_{o1} \parallel r_{o2})$$

→ High gain (M_1, M_2 sat)→ High Swing (V_b is high)

... How to make it more linear.

Source degeneration

$$G_m = \frac{g_m}{1+g_m R_s}$$

→ Lower gain but much more linear.

Solid state Equations

$$n = N_c e^{\frac{E_F - E_c}{kT}} \quad p = N_v e^{\frac{E_v - E_F}{kT}} \quad np = n_i^2 \quad E_F = \frac{E_c + E_v}{2}$$

Drift

$$\vec{J} = \vec{J}_n + \vec{J}_p = q(\mu_n n + \mu_p p) \vec{E}$$

Diffusion


$$\vec{J} = -qD \frac{dP}{dx} \quad ; \quad \frac{D}{\mu} = \frac{kT}{q}$$

Barrier potential (PN)

$$\phi_0 = \frac{1}{2} \frac{q N_A}{\epsilon_s} x_p^2 \left(1 + \frac{N_A}{N_D} \right)$$

$$C_{j0} = \left[\frac{q \epsilon_s}{2 \left(\frac{1}{N_A} + \frac{1}{N_D} \right) \phi_0} \right]^{1/2}$$
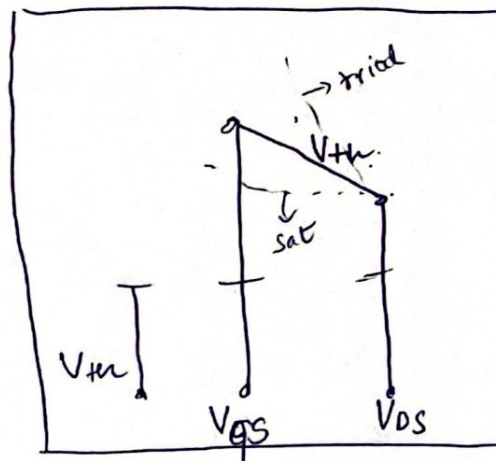
$$C_j = \frac{C_{j0}}{\sqrt{1 - \frac{V_D}{\phi_0}}}$$



MOSFET

$$V_{TH} = \phi_T + \Delta\phi_{ox} \quad \text{where} \quad \phi_T = \frac{2kT}{q} \ln \frac{N_D}{N_A}$$

$$V_{TH} = V_{FB} + 2\phi_F + \gamma \sqrt{2\phi_F} \quad \text{where} \quad \gamma = \frac{\sqrt{2q\epsilon_s N_D}}{C_{ox}}$$

$$V_{TH} = V_{TH0} + \gamma \left[\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F} \right] \quad \phi_F = \frac{\phi_T}{2}$$

Body effect

Circuits (calculate g_m then proceed) (Equate currents)

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2 \right] \quad \text{Triode}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad \text{Sat}$$

$$g_{mb} = \chi g_m = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}} g_m \rightarrow \gamma = \frac{\sqrt{2q\epsilon_s N_D}}{C_{ox}}$$

in saturation intrinsic gain

$$g_{mro} = \frac{4I_D}{\mu_n C_{ox} (V_{GS} - V_{TH})^3 \frac{W}{L}}$$

$$\lambda = \frac{1}{L'} \frac{\partial I_D}{\partial V_{DS}} = \frac{1}{V_P}$$

$$\lambda = \frac{1}{r_o I_D} ; r_o = \frac{V_A}{I_D}$$

L if channel length is doubled

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \frac{2 I_D}{(V_{GS} - V_{TH})}$$

small signal

$$r_o = \frac{1}{\lambda I_D} \quad (\text{saturation})$$

large signal







$$r_o = \frac{1 + \lambda V_{DS}}{\lambda I_D}$$

$$V_{in} = V_{TH} + \left(\frac{2 I_D}{\mu_n C_{ox} \left(\frac{W}{L} \right)} \right)^{1/2}$$

$$R_o^{-1} = \frac{\partial I_D}{\partial V_{DS}} \quad (\text{triode})$$

$$\begin{aligned} & 850 \frac{8.85 \times 10^{-14} \left(\frac{Cox}{F/m^2} \right)}{\mu_n Cox \frac{W}{L}} = 1.34225 \times 10^{-4} \\ & 100 \mu_p Cox = 3.835 \times 10^{-5} \end{aligned}$$

Intrinsic NMOS

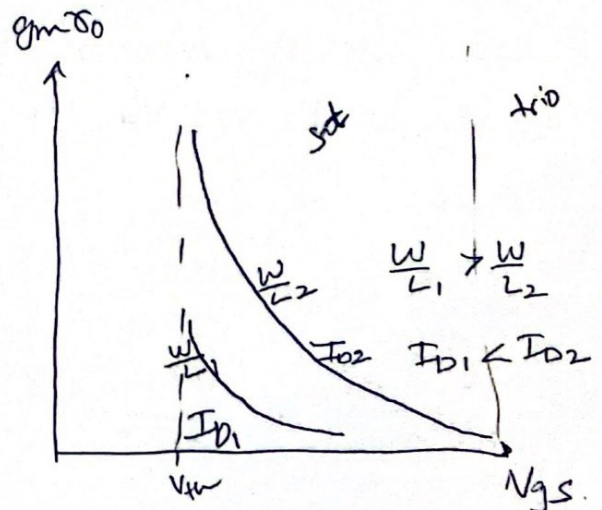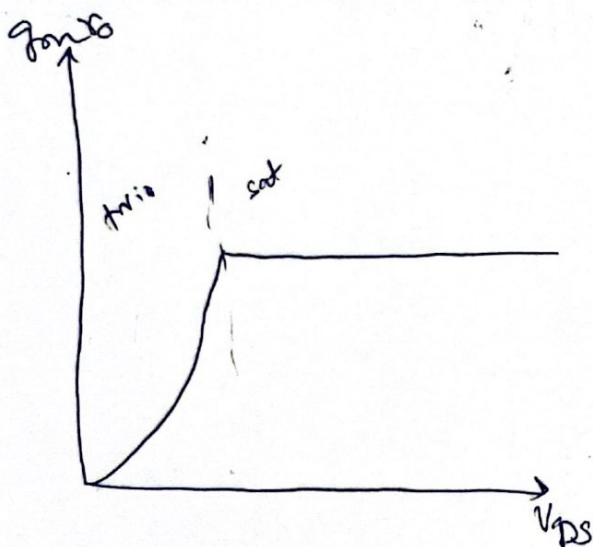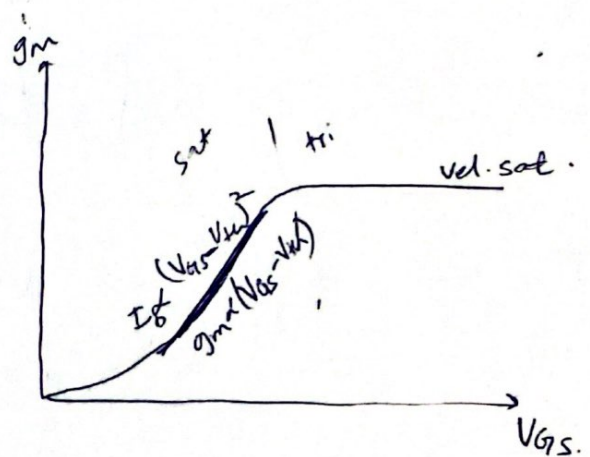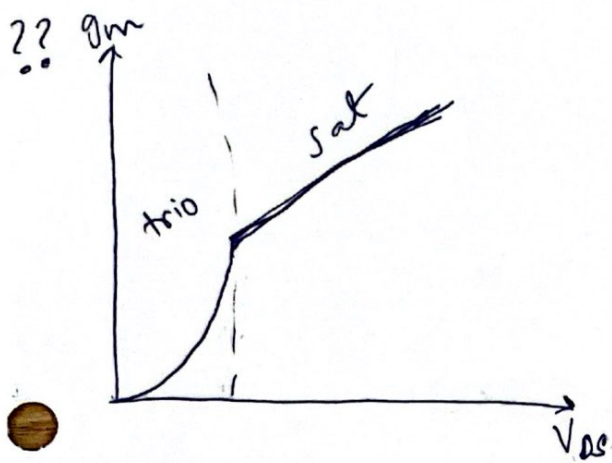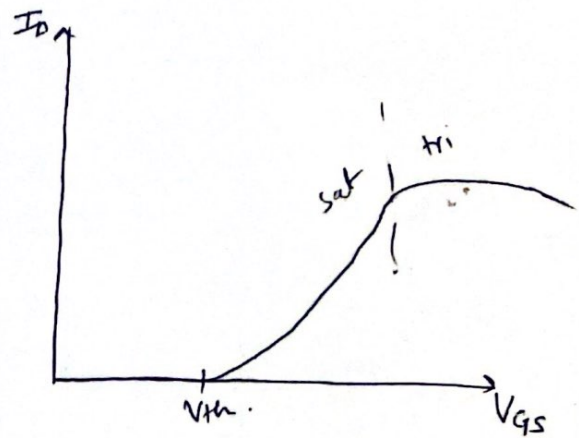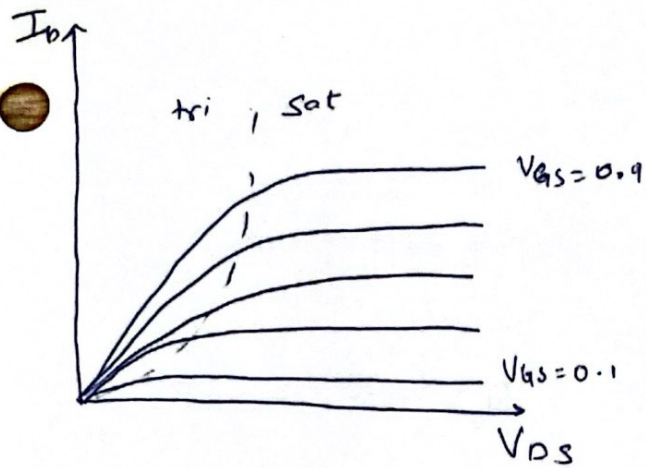

gm diode

$$g_m = \mu_n C_{ox} \left(\frac{W}{L} \right) V_{DS} (1 + \lambda V_{DS})$$

$$r_o^{-1} = g_o = \frac{\partial I_D}{\partial V_{DS}} = \mu_n C_{ox} \left(\frac{W}{L} \right) \left\{ (V_{GS} - V_{th} - V_{DS}) (1 + \lambda V_{DS}) + \lambda [(V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2}] \right\}$$

$$A_v = -g_m r_o$$

Equivalent circuits

G_m:- Short V_{out}, find $\frac{i_{out}}{V_{in}}$. $g_m = \frac{\partial I_D}{\partial V_{GS}}$

R_{out}:- $R_{out} = \frac{V_t}{i_t}$; short V_{in} ; apply test V_{in} & find $\frac{V_{in}}{i_{in}}$

R_{in}:- $R_{in} = \frac{V_t}{i_t}$; short V_{out} ; apply test V_{in} & find $\frac{V_{in}}{i_{in}}$

$$V_{th} = V_{th0} + \gamma \left[\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F} \right]$$

$$I_x = C \frac{dV_x}{dt} \Rightarrow dV_x = \frac{1}{C} \cdot I_x dt$$
$$\int dV_x = \frac{1}{C} \int_0^t I_x dt$$

- ① → Figure out Sat. vs. triode vs. off → Write down Eqs.
② → When does it move to Tri/sat.
③ → What is I_x vs. V_x etc...

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \left[2 V_{DS} \right]$$

Circuits → CS, CO, CS^{cascode}, mirror, current mirrors, 3 appendices.

$$V_{th0} = 2\phi_F + \gamma \sqrt{2\phi_F}$$

$$V_{th} = V_{th0} + \gamma \left(\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F} \right) \quad \text{Body Effect}$$

$$\phi_F = \frac{kT}{q} \ln \frac{N_D}{n_i}$$

$$\gamma = \frac{\sqrt{2q\epsilon_{Si}N_D}}{C_{ox}}$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

TRIODE

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \left[2(V_{GS} - V_{th})V_{DS} - V_{DS}^2 \right]$$

SATURATION

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \left[V_{GS} - V_{th} \right]^2 \left[1 + \lambda V_{DS} \right]$$

$$g_m = \mu_n C_{ox} \frac{W}{L} \left[V_{GS} - V_{th} \right] \left[1 + \lambda V_{DS} \right]$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \left[1 + \lambda V_{DS} \right]$$

$$g_m = \frac{2 I_D}{V_{GS} - V_{th}}$$

Channel length modulation

$$\lambda = \frac{1}{L'} \frac{\partial x_d}{\partial V_{DS}}$$

$$\lambda = \frac{\text{Small signal}}{r_o I_D}$$

$$r_o = \frac{1}{\lambda I_D}$$

Large signal

$$r_o = \frac{1 + \lambda V_{DS}}{\lambda I_D}$$

$$r_o = \frac{\partial I_D}{\partial V_{DS}}$$


Body effect

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} = \chi g_m$$

$$\text{where } \chi = \frac{\gamma}{2\sqrt{2\phi_F + V_{th}}}$$

$$\gamma = \frac{\sqrt{2q\epsilon_{Si}N_D}}{C_{ox}}$$

Small signal model

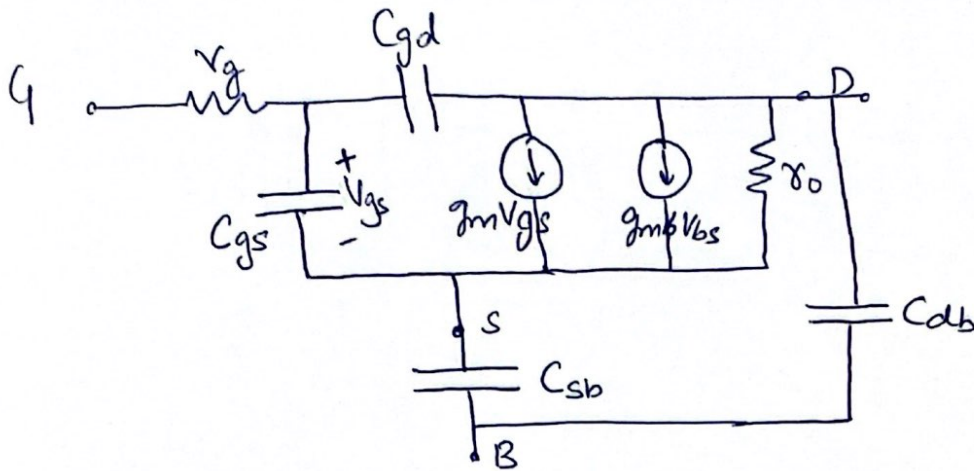

$$f_T = \frac{1}{2\pi} \frac{g_m}{C_{gs} + C_{gd}}$$

f_T is limited by $V_{sat} \Rightarrow$ By architecture


Capacitances	C_{gb}	C_{gd}	C_{gs}
Cutoff	$W L_{eff} C_{ox}$	$W C_{ov}$	$W C_{ov}$
Linear/Triode	0	$W C_{ov} + \frac{W L_{eff} C_{ox}}{2}$	$W C_{ov} + \frac{W L_{eff} C_{ox}}{2}$
Saturation	0	$W C_{ov}$	$W C_{ov} + \frac{2}{3} W L_{eff} C_{ox}$

At low frequencies

$$C_{gs} = \frac{2}{3} C_{ox} W L_{eff} + C_{ov} W$$

$$C_{gd} = C_{gd0} \cdot W$$

$$C_{db}$$

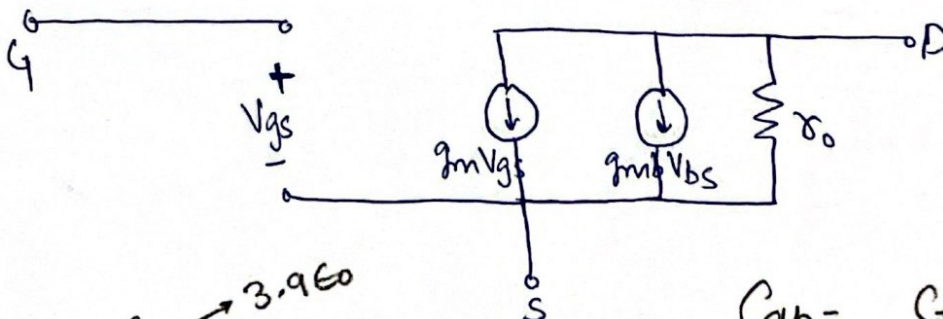

$$\begin{aligned} G_n &= 0.56 \times 10^{-3} \\ G_p &= 0.94 \times 10^{-3} \\ C_{sw_n} &= 0.35 \times 10^{-11} \\ C_{sw_p} &= 0.32 \times 10^{-11} \end{aligned}$$

$$C_{ox} = \frac{\epsilon_{SiO_2}}{t_{ox}} \rightarrow 3.9 \epsilon_0$$


$$\begin{aligned} L_{eff} &= L - 2(L_{ov}) \\ C_{ov} &= C_{ox} \times L_{ov} \end{aligned}$$

$$\begin{aligned} V_D &= 1 \\ P_B &= 0.9 \\ M_J &= 0.6 \\ M_{JSW} &= 0.2 \end{aligned}$$

$$\begin{aligned} C_{db} &= \frac{C_J \times W \times 1.5 \mu m}{\left[1 - \frac{V_D}{P_B}\right]^{M_J}} \\ &+ \frac{C_{JSW} (2W + 3 \mu m)}{\left[1 - \frac{V_D}{P_B}\right]^{M_{JSW}}} \end{aligned}$$

Common Source (Gate -1/p ; Drain 1/p)

I Basic

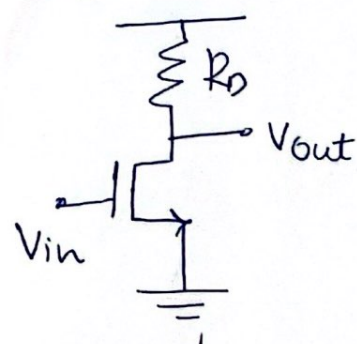


$$A_v = -g_m R_D \quad \lambda = 0$$

$$A_v = -g_m (R_D \parallel r_o) \quad \lambda \neq 0$$


$$R_{in} = \infty$$

$$R_{out} = R_D \parallel r_o$$

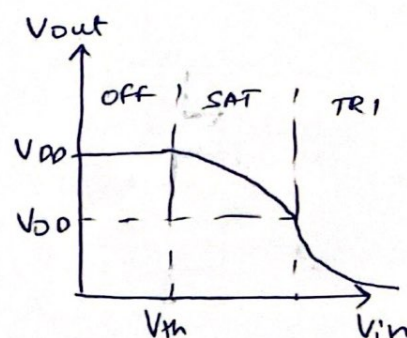

- High gain
- Nonlinear
- High R_{in} , low R_{out}

II Diode connected

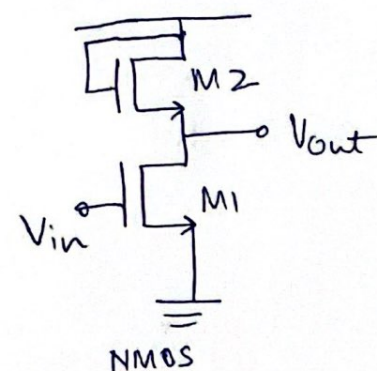


$$A_v = \frac{-g_{m1}}{g_{m2}} = - \sqrt{\frac{(W/L)_1}{(W/L)_2}} \times \frac{1}{1 + \chi_2} \quad \chi = \frac{\gamma}{2\phi_F + V_{SB}}$$

$$R_{in} = \infty$$

$$R_{out} = r_{o1} \parallel \left\{ \frac{1}{g_{m2} + g_{mb2} + \frac{1}{r_{o2}}} \right\} \rightarrow \frac{1}{g_{m2} + g_{mb2}} \parallel r_{o2} \parallel r_{o1}$$


- More linear!
- lower gain!

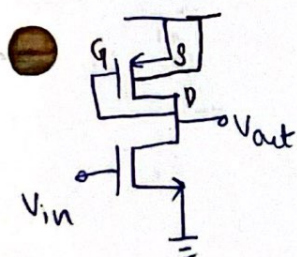



$$A_v = - \sqrt{\frac{\mu_n}{\mu_p} \frac{(W/L)_1}{(W/L)_2}}$$

→ No body effect

III Active load

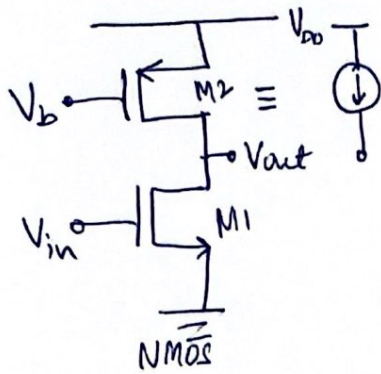

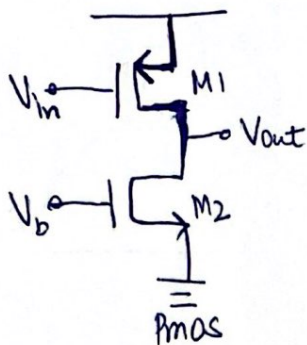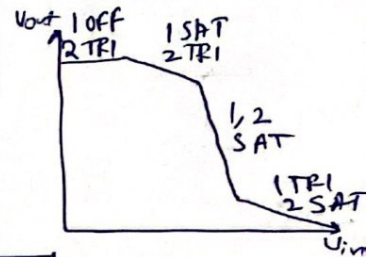
$$\begin{aligned} A_v &= -g_{m1} (Y_{o1} \parallel Y_{o2}) \\ R_{in} &= \infty \\ R_{out} &= Y_{o1} \parallel Y_{o2} \end{aligned}$$



$$\begin{aligned} A_v &= -g_{m1} (Y_{o1} \parallel Y_{o2}) \\ R_{in} &= \infty \\ R_{out} &= Y_{o1} \parallel Y_{o2} \end{aligned}$$

→ High gain
→ High swing. } Not so linear.

IV Source degeneration

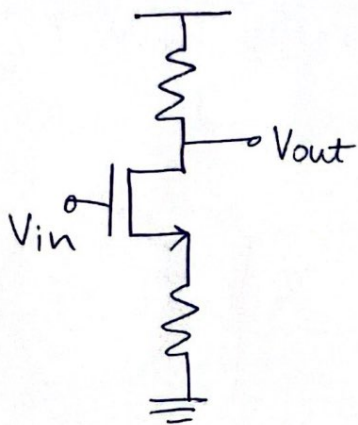

$$A_v = \frac{-R_D}{\frac{1}{g_m} + R_S} \quad \lambda = 0; g_{mb} = 0$$

$$A_v = -G_m R_{out} \quad \lambda \neq 0; g_{mb} \neq 0$$

$$G_m = \frac{g_m}{1 + (g_m + g_{mb} + \frac{1}{r_o}) R_S} = \frac{g_m r_o}{r_o + (g_m + g_{mb} + 1) R_S}$$

$$R_{out} = [r_o (1 + (g_m + g_{mb}) R_S) + R_S] \parallel R_D$$


$$R_{in} = \infty$$

→ lower gain
→ Much more linear.

$$\begin{aligned} R_{out} &\approx (1 + g_m r_o) R_S + r_o \\ &\approx (1 + g_m R_S) r_o + R_S \end{aligned}$$

Common Drain (or) Source follower

[Gate i/p ; Source o/p]

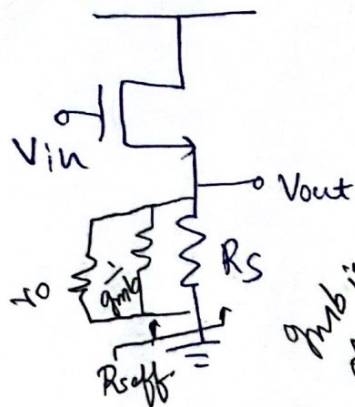

g_{mb} is just a resistor of value $\frac{1}{g_{mb}}$ in this case because drain is short $\Rightarrow R_{seff} = \frac{1}{g_{mb}} || R_S || r_o$

$$A_v = \frac{R_{seff}}{\frac{1}{g_m} + R_{seff}}$$

$$R_{seff} = R_S || r_o || \frac{1}{g_{mb}}$$

$\rightarrow$ No $\frac{1}{g_m}$ in this.


$$A_v = \frac{1}{1 + X} \text{ when } R_S \gg \frac{1}{g_{mb}}$$

$$R_{out} = \frac{1}{g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_S}} \approx \frac{1}{g_m + g_{mb}}$$

$R_{in} = \infty$ R_{seff} is resistance looking from ground into the source.

- $\rightarrow$ High R_{in}
- $\rightarrow$ Low R_{out} } Buffer.
- $\rightarrow$ Maybe used as a level shifter as well

Common Gate [Source i/p ; Drain output]

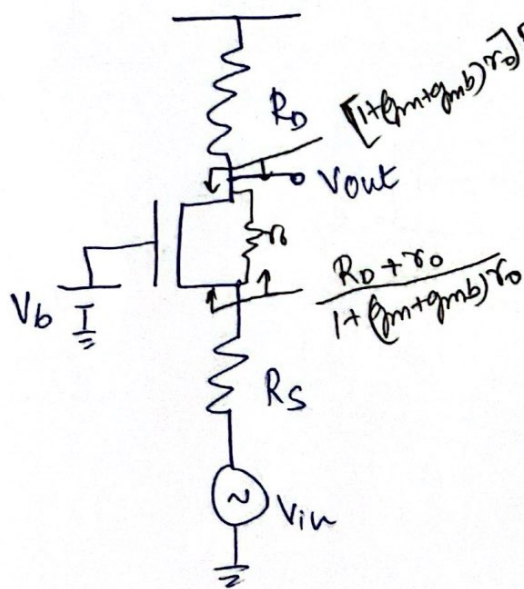

$$A_v = +g_m R_D (1 + X) \quad \lambda = 0 ; R_S = 0$$

$$A_v = \frac{(g_m + g_{mb}) \frac{r_o}{1 + (g_m + g_{mb}) r_o} R_D R_S}{R_D + r_o + R_S (1 + (g_m + g_{mb}) r_o)} \quad \lambda \neq 0, R_S \neq 0$$

$$R_{in} = R_S + \frac{r_o + R_D}{1 + (g_m + g_{mb}) r_o} \quad \text{Body effect decreases } R_{in}$$

$$R_{out} = R_D || \{ r_o + (1 + g_m r_o) R_S \}$$



Same as source degen.

- $\rightarrow$ High R_{out}
- $\rightarrow$ Low R_{in} } Impedance matching



Cascode

I Current sources

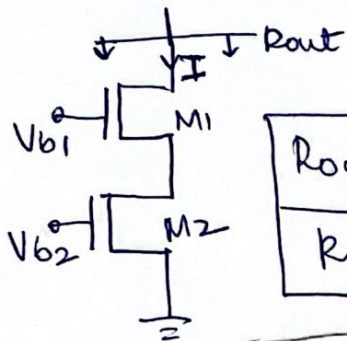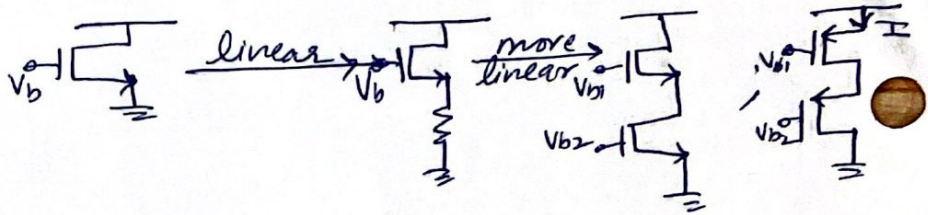


$$R_{out} = (1 + g_{m1} r_{o1}) r_{o2} + r_{o1}$$


$$R_{out} \approx (g_{m1} r_{o1}) r_{o2}$$

II

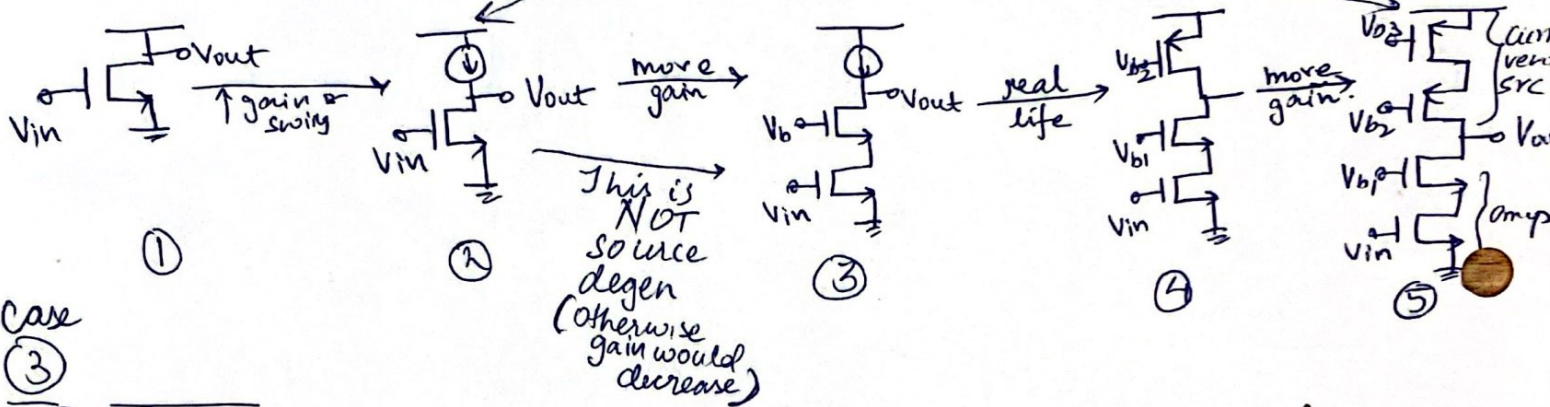Cascode amplifiers Rout booster → High Q_p resistance



Case (3)

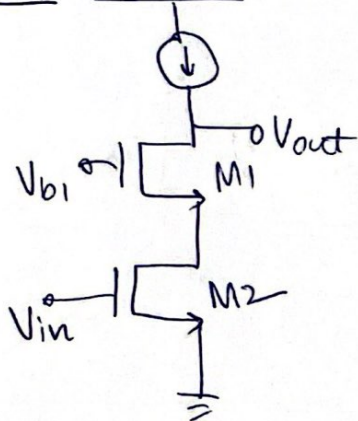

Case (5)

$$R_{out} = (1 + g_{m1} r_{o1}) r_{o2} + r_{o1}$$

$$G_M \approx g_{m2}$$

$$A_v = -G_M R_{out}$$

$$G_M = g_{m2} \cdot \frac{r_{o2}}{r_{o2} + \frac{1}{g_{m1} + g_{m5}} \parallel r_{o1}}$$

Biassing

$$V_{in} > V_{th1}$$


$$V_{out} > V_{oD1} + V_{oD2}$$

op swing decreases by V_{oD2}


$$R_{out} = [(1 + g_{m3} r_{o3}) r_{o4} + r_{o3}] \parallel [(1 + g_{m1} r_{o1}) r_{o2} + r_{o1}]$$

$$G_M = g_{m2}$$


$$A_v = -G_M R_{out}$$

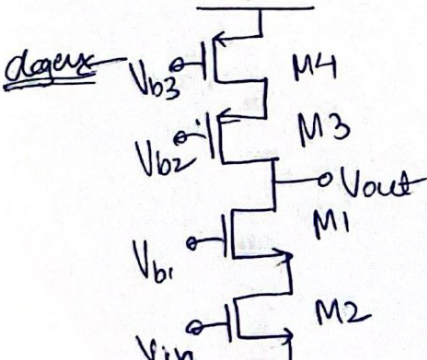

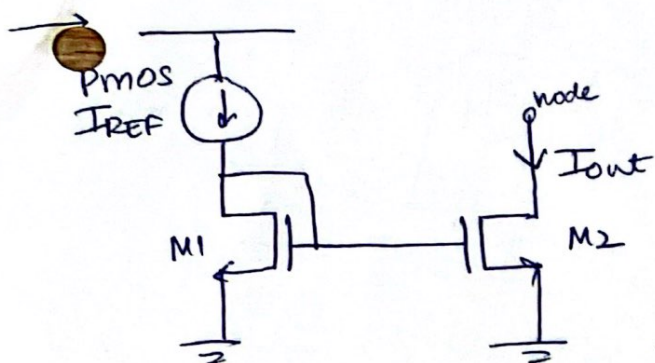Current Mirrors (To bias) { Ignoring CLM }



PMOS I_{REF} $\rightarrow$ NMOS bias

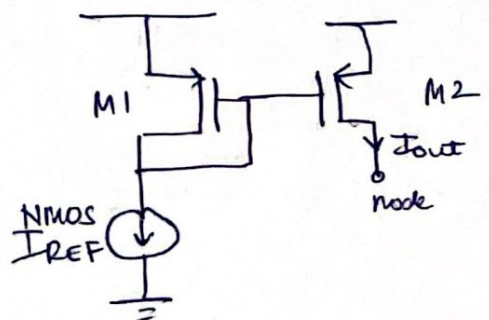


NMOS I_{REF} $\rightarrow$ PMOS bias.

$$I_{out} = \left\{ \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} \right\} I_{REF}$$


Series $\Rightarrow L \times 2$ $\odot$ $W \div 2$

Parallel $\Rightarrow L \div 2$ $\odot$ $W \times 2$

NMOS SRC $\rightarrow$ NMOS bias

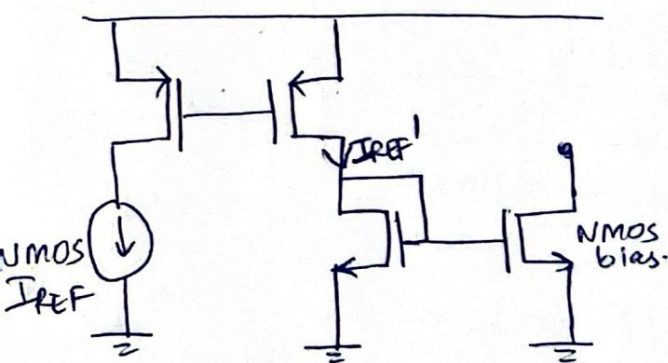


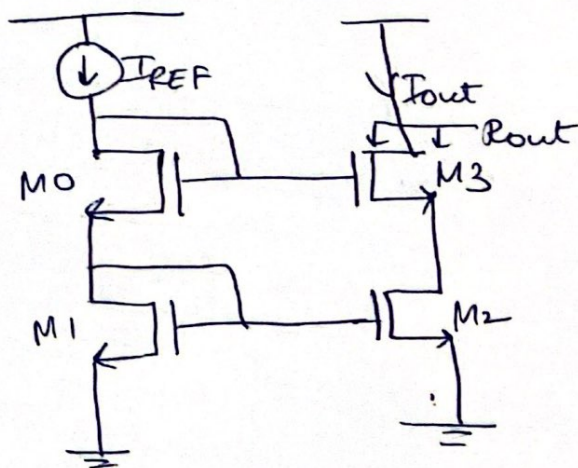If we do not ignore CLM we must use cascode to ensure $I_{REF} = I_{out}$




$\rightarrow$ M0 is to properly bias M3 and M3 is to ~~reduce~~ ^{reduce} CLM because it increases R_{out} & I_{out} doesn't change as much. This design requires very high V_{DD} ~~low~~ values.

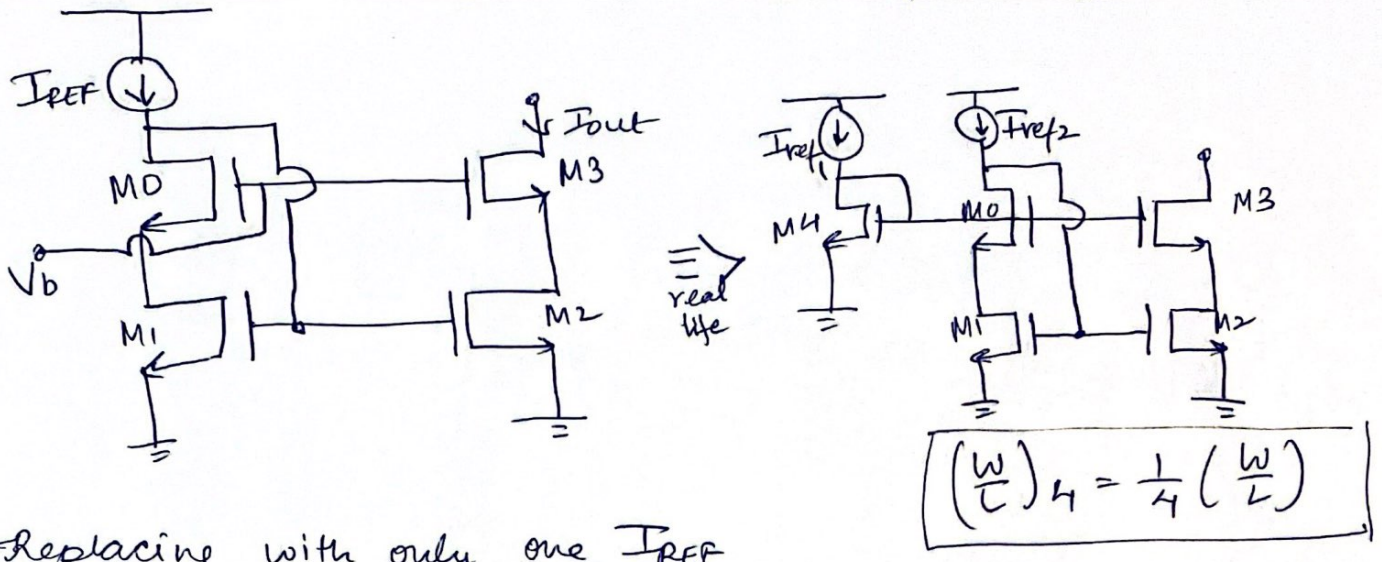→ To lower bias values & increase $V_{peak(min)}$




→ Replacing with only one I_{REF}

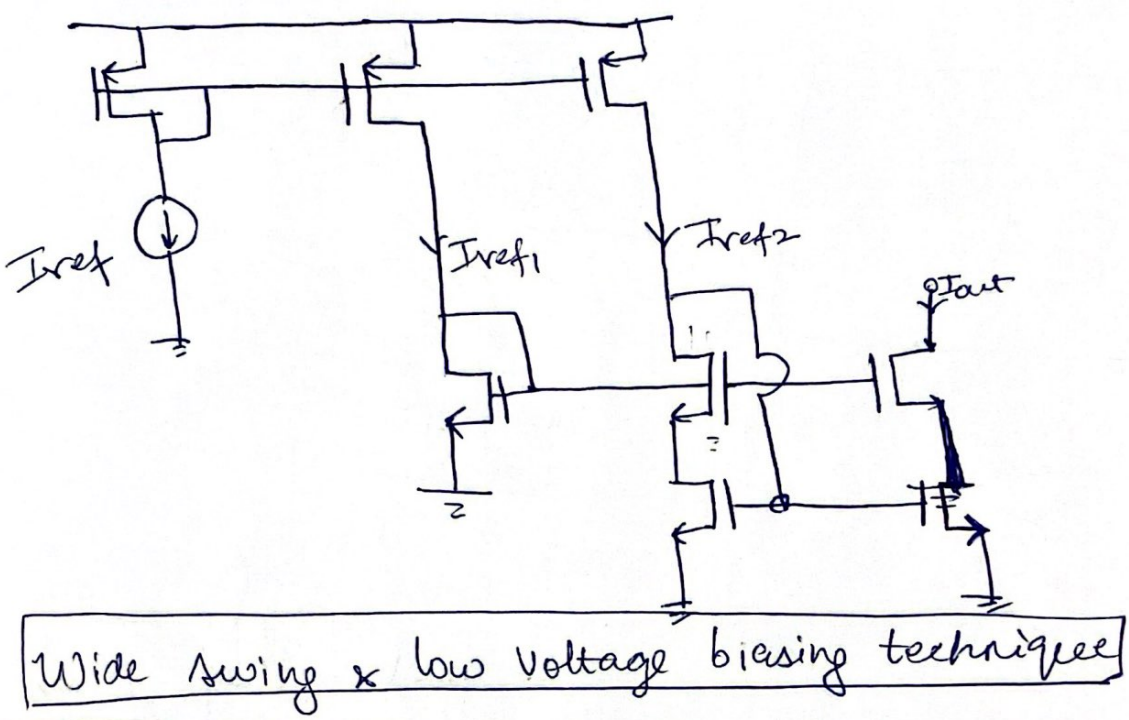


Basic Rules for solving any amplifier circuit

Step a

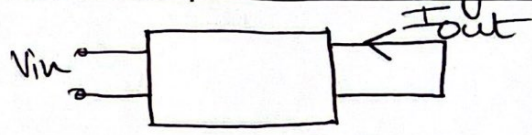

- Short Q_p to GND.
- Short all DC sources
- Find $\frac{I_{out}}{V_{in}} = G_m$


Step b

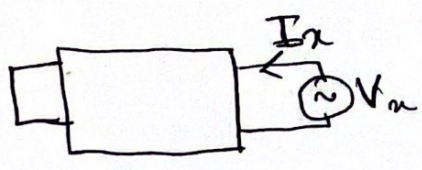






- Remove all independent sources including V_{in}
- Find $R_x = \frac{V_x}{I_x}$

$$A_v = -G_m R_x$$

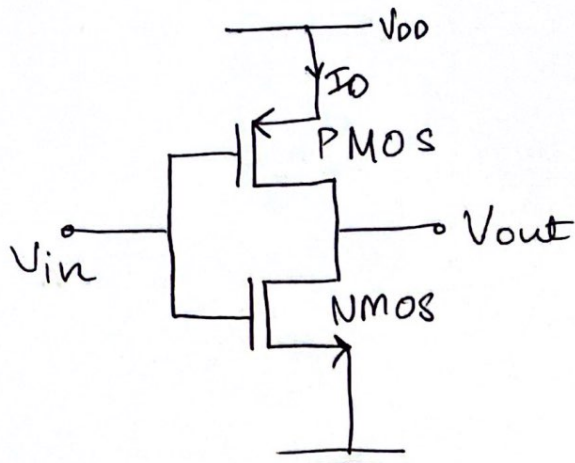
MOS Inverter → This is called active load!






$$A_v = -(g_{m_n} + g_{m_p})(r_{on} || r_{op})$$

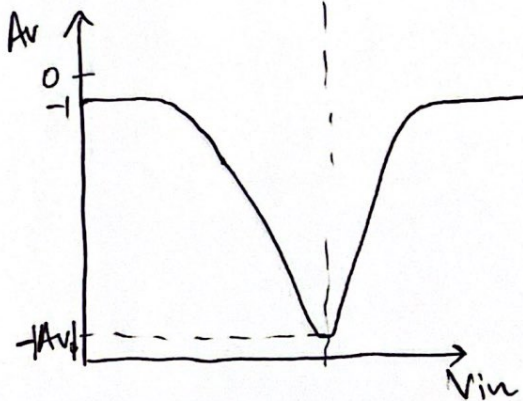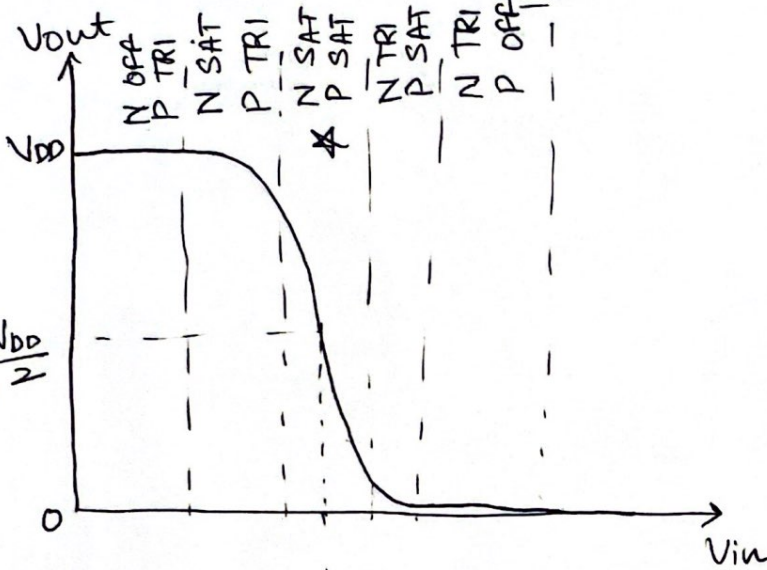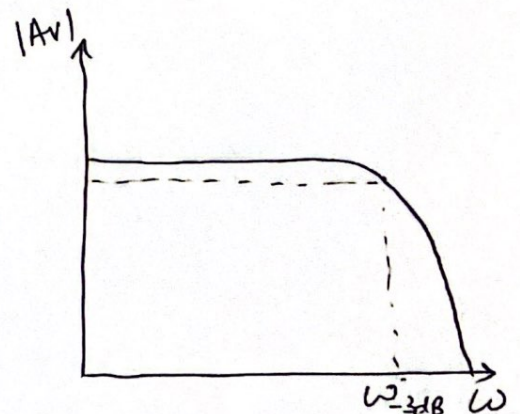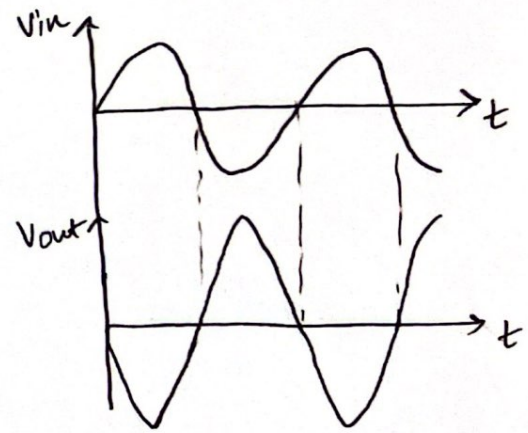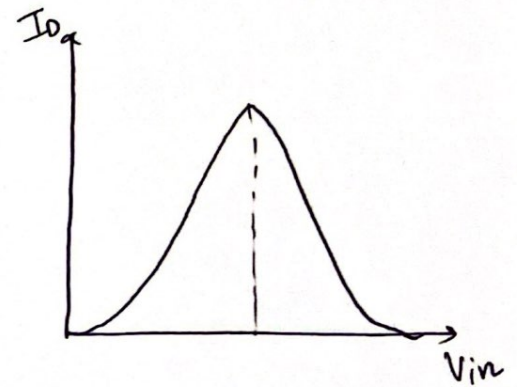


Small signal model

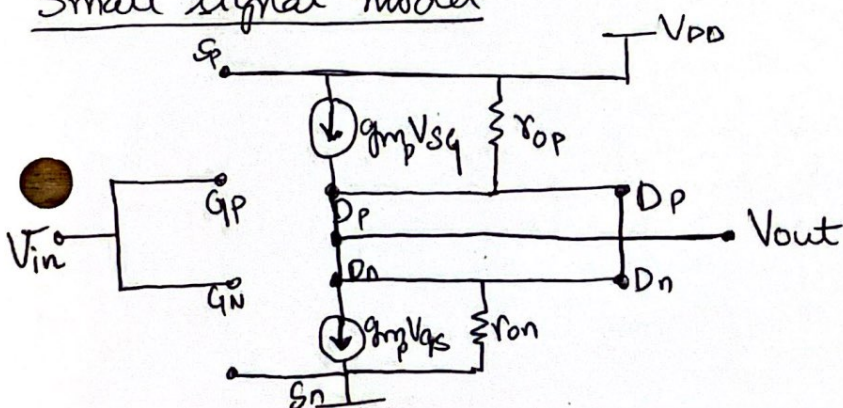


Resistance Equivalents

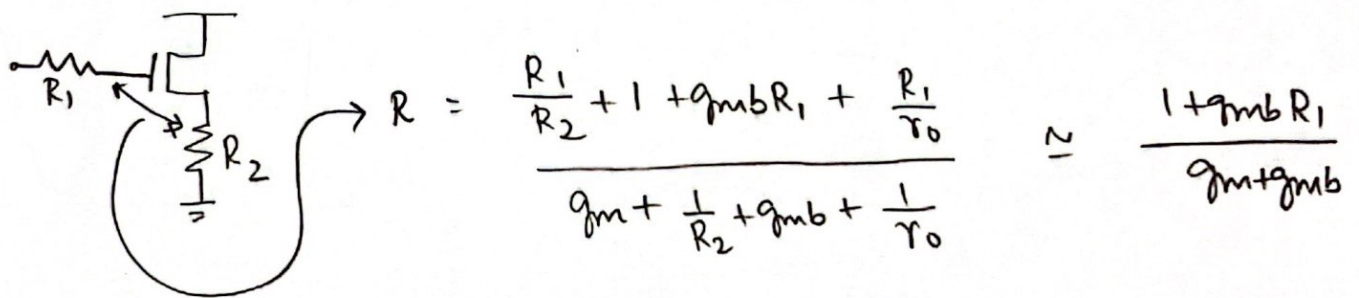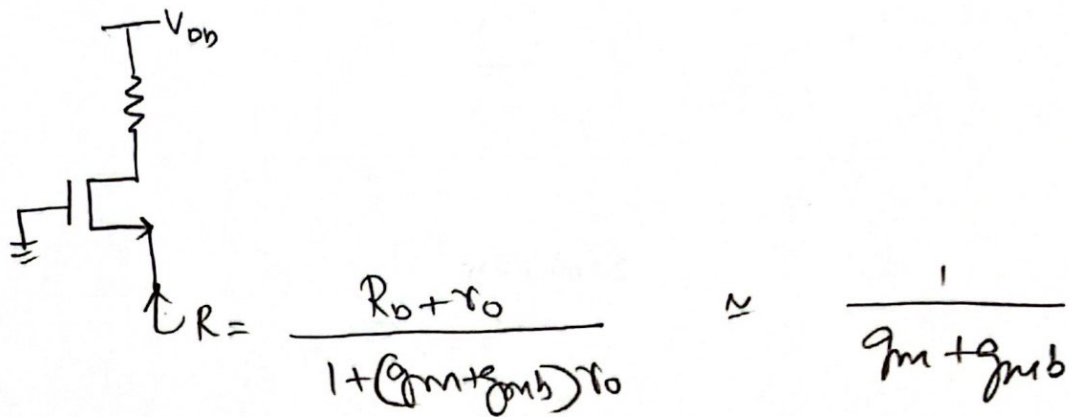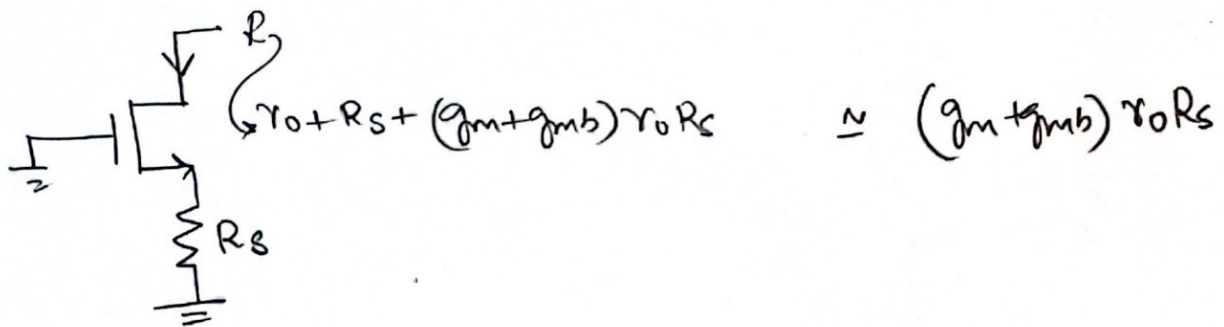

MOSFET Summary.

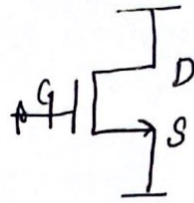

π model

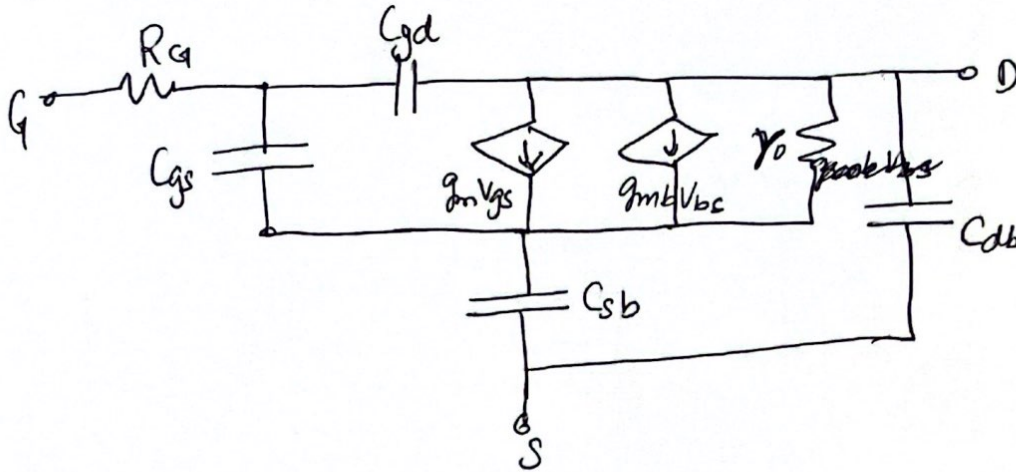

$$I_{D_{\text{triode}}} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$I_{D_{\text{sat}}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS}) \quad \lambda = \frac{1}{V_A}$$


$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) \quad g_{mb} = \chi g_m, \quad \chi = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}}$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{(V_{GS} - V_{th})}$$


$$r_o = \frac{1}{\lambda_n I}$$

BJT Summary.

Small signal model.

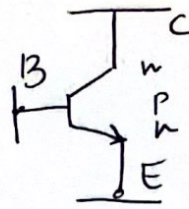

II

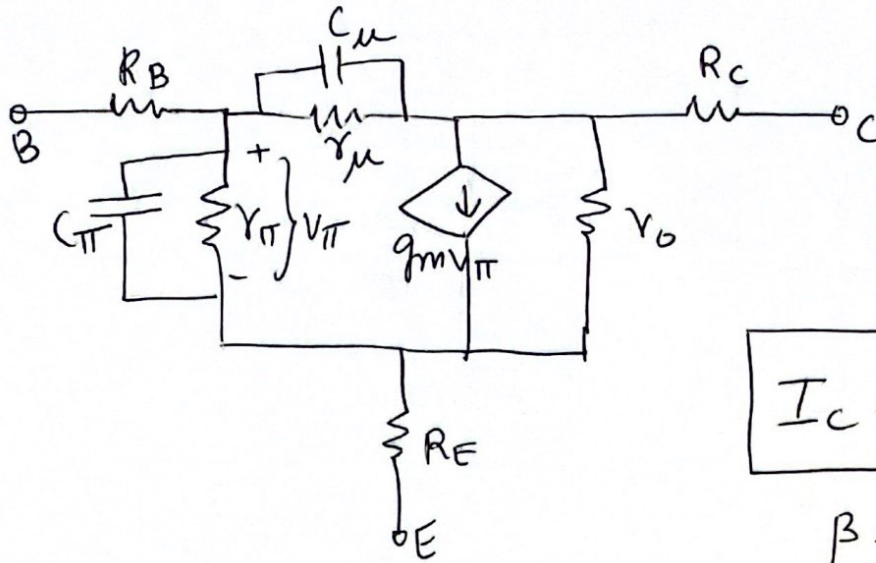


$$I_C = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right)$$

$$\beta = \frac{\alpha}{\alpha - 1} ; \frac{1}{\alpha} - \frac{1}{\beta} = 1$$

T model

$\alpha \sim 1$
 $\beta \sim 100$

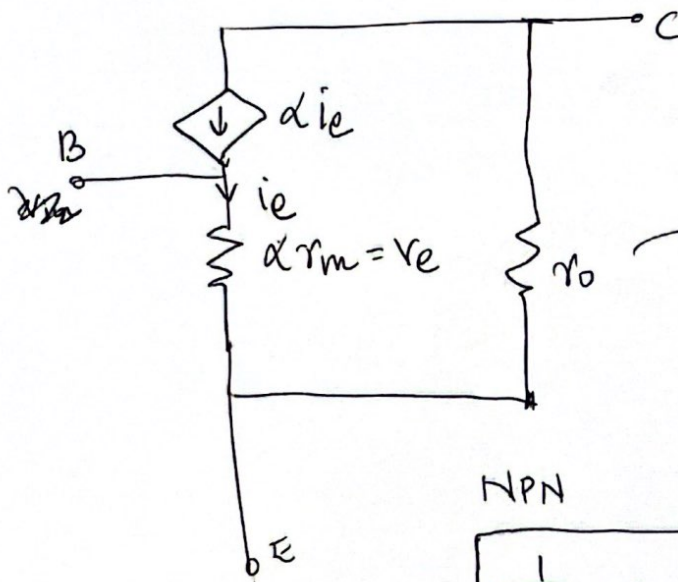

$$I_C = \beta I_B$$

$$I_C = \alpha I_E$$

$$I_C = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$

Early Effect

$$\frac{1}{r_m} = g_m = \frac{I_{C,Q}}{V_T} = \frac{I_C}{V_{be}}$$

$$r_{\pi} = \frac{\beta}{g_m} = \beta r_m$$

$$\left[\frac{\partial I_B}{\partial V_{BE}} \right]^{-1}$$


$$r_o = \frac{V_A}{I_{C,Q}}$$

$$\left[\frac{\partial I_C}{\partial V_{CE}} \right]^{-1}$$


$$r_{\mu} = \left[\frac{\partial I_B}{\partial V_{CB}} \right]^{-1}$$

$$r_{\mu} \approx \beta r_o$$

PMOS

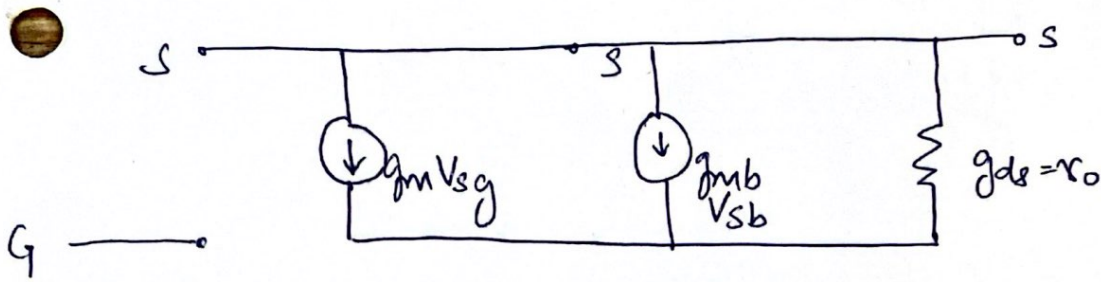

(a)

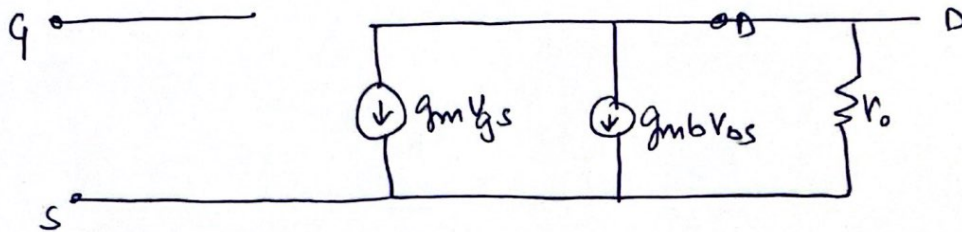

TRIODE

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} \left[2(V_{GS} - V_{th}) V_{DS} - V_{DS}^2 \right]$$

$$V_{GS} < V_{th}$$

$$V_{DS} > V_{GS} - V_{th}$$

SAT

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} \left[V_{GS} - V_{th} \right]^2 \left[1 + \lambda V_{DS} \right]$$

$$V_{GS} < V_{th}$$

$$V_{DS} \leq V_{GS} - V_{th}$$

Laplace Transform

$$L[f(t)] = \int_0^{\infty} f(t) e^{-st} dt = F(s) \quad ; \quad s = \sigma + j\omega$$

$$\delta(t) \text{ ————— } 1$$

$$1 \text{ ————— } \frac{1}{s}$$

$$t \text{ ————— } \frac{1}{s^2}$$

$$t^n \text{ ————— } \frac{n!}{s^{n+1}}$$

$$t^a \text{ ————— } \frac{\Gamma(a+1)}{s^{a+1}}$$

$$e^{-at} \text{ ————— } \frac{1}{s+a}$$

$$\cos \omega t \text{ — } \frac{s}{s^2 + \omega^2}$$

$$\sin \omega t \text{ — } \frac{\omega}{s^2 + \omega^2}$$

$$L[f'(t)] = sL[f(t)] - f(0)$$

$$L[f''(t)] = s^2 L[f(t)] - sf(0) - f'(0)$$

$$L\left[\int f(t') dt'\right] = \frac{1}{s} L[f(t)]$$

differential $\Rightarrow \times s$ - something

integral $\Rightarrow \div s$

$$L[e^{at} f(t)] = F(s-a)$$

$$y(t) = x(t) * h(t) \quad \left. \begin{array}{l} \text{For} \\ \text{LT} \end{array} \right\} \Rightarrow Y(s) = H(s) \cdot X(s)$$

Inverse

$$f(t) = L^{-1}[F(s)] = \frac{1}{2\pi i} \lim_{t \rightarrow \infty} \int_{\sigma-j\infty}^{\sigma+j\infty} F(s) e^{st} ds$$

→ Converts a differential equation to an algebraic equation.



Frequency Response { 3 methods, CD, CS, Cascode, Cascade, BJT enhancement mod, Diff pair,

(I) Direct approach

- > Draw small signal model with the caps.
- > Solve KVL and KCL to find $\frac{V_{out}(s)}{V_{in}(s)} = A_v(s)$
- > Find poles and zeroes (ω_p, ω_z)
- > Make assumptions to solve for ω_p if needed.
 $\omega_{p1} \ll \omega_{p2}$; $C_{gs} \gg C_{gd}(1+g_m R_o)$; $g_m R_o \gg 1$.

Note:- ω_z is usually very high so it can be ignored.

Common Source

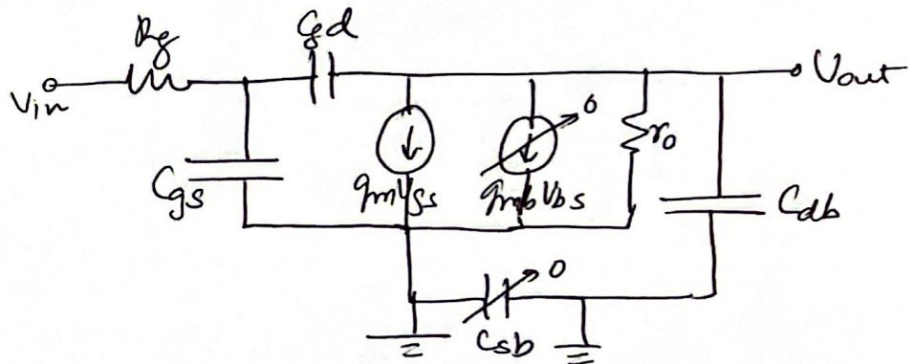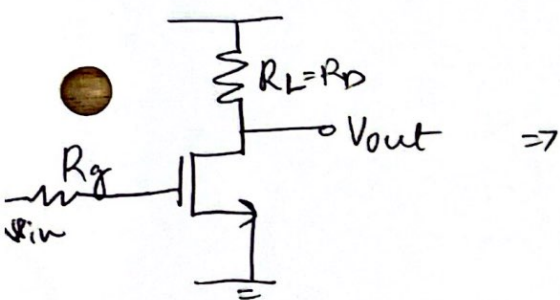

$$A_v(s) = \frac{s(C_{gd} - g_m)R_o}{R_g R_o (C_{gs} C_{gd} + C_{gs} C_{db} + C_{gd} C_{db})s^2 + [R_g (1 + g_m R_o) C_{gd} + R_g C_{gs} + R_o (C_{gd} + C_{db})]s + 1}$$

$$\omega_z = \frac{g_m}{C_{gd}} \quad ; \quad \text{Assume } \omega_{p1} \ll \omega_{p2}$$

$$\omega_{p1} = \frac{1}{R_g (1 + g_m R_o) C_{gd} + R_g C_{gs} + R_o (C_{gd} + C_{db})}$$

$$\omega_{p2} = \frac{R_g (1 + g_m R_o) C_{gd} + R_g C_{gs} + R_o (C_{gd} + C_{db})}{R_g R_o (C_{gs} C_{gd} + C_{gd} C_{db} + C_{gs} C_{db})}$$

Annotations for pole simplification:

- For ω_{p1} , $C_{gs} \gg C_{gd}(1+g_m R_o)$ and $g_m R_o \gg 1$, so $\omega_{p1} \approx \frac{1}{R_o (C_{gd} + C_{db})}$.
- For ω_{p2} , $g_m R_o \gg 1$, so $\omega_{p2} \approx \frac{g_m}{C_{gs} (1 + \frac{C_{db}}{C_{gd}})}$.

→ A simpler direct approach

> Assume no zeroes:- $A_v(s) = \frac{A_{v0}}{(\tau_{p1}s+1)(\tau_{p2}s+1)\dots(\tau_{pn}s+1)}$

> $D(s) = b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0$

$b_1 = \sum_{i=1}^n \tau_{pi} ; b_0 = 1$

Dominant pole assumption:- $\Rightarrow$ only b_1, b_0 affect ω_{-3dB}

$\therefore D(s) \approx b_1 s + b_0 = b_1 s + 1$

$\therefore \boxed{\omega_{-3dB} \approx \frac{1}{b_1} \approx \frac{1}{\sum \tau_p}}$

②

Open circuit time constant method

> Find R_{jo} facing capacitor C_j when all other caps are open removed.

> $\tau_{jo} = R_{jo} C_j \quad ; \Rightarrow \boxed{\omega_{-3dB} = \frac{1}{\sum_{j=1}^n R_{jo} C_j}}$

> For a cap with gate & drain on two sides

$R = R_{left} + R_{right} + g_m R_{left} R_{right}$

For common source

$\omega_{-3dB} = \frac{1}{R_g (1 + g_m R_D) C_{gd} + R_g C_{gs} + R_D (C_{gd} + C_{db})}$




Associating poles to nodes

Assign a pole to each node and find RC time constant

$$\omega = \frac{1}{\sum RC}$$

Miller effect

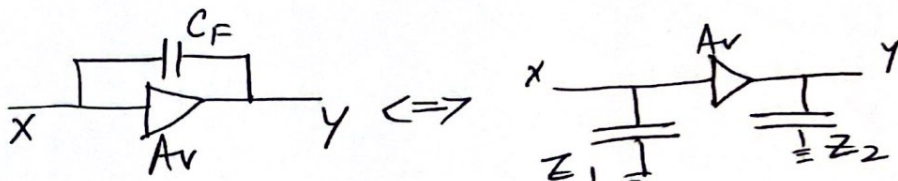

$$Z_1 = \frac{Z}{1 - A_v}$$

$$Z_2 = \frac{Z}{1 - \frac{1}{A_v}}$$

where $Z = \frac{1}{sC_F}$

$$\Rightarrow C_{F1} = C_F (1 - A_v)$$

$$\Rightarrow C_{F2} = C_F \left(1 - \frac{1}{A_v}\right)$$

Two stage.

Coupling caps lower bandwidth by introducing an $\omega_{zab}(\text{low})$

To find $\omega_{zab}(\text{low})$ use $A_v(s) = \frac{K_n s^n}{(s+s_1)(s+s_2)+\dots+(s+s_n)}$

Approximating to dominant pole

$$A_v(s) = \frac{K_n s}{s + \sum_{i=1}^n s_i}$$

and

$$\omega_{zab} = \sum_{i=1}^n s_i$$



Recipe!

Find R_{is} facing the capacitor C_i when all other caps are short (because they are at higher frequencies).

$$\omega_{zablow} = \sum_{i=1}^n \frac{1}{R_{is} C_i}$$

C_i are caps contributing to the lower ω_{zab} .

Common Drain

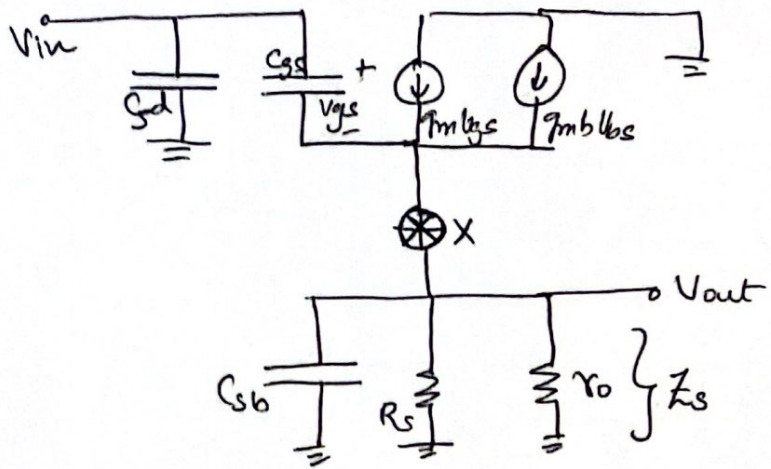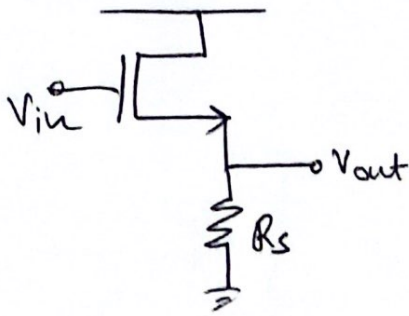



Direct method

$$A_v = \frac{S C_{gs} + g_m}{S C_{gs} + \frac{1}{Z_s} + g_m + g_{mb}}$$

$$S_z = \frac{-g_m}{C_{gs}}$$

$$S_p = \frac{-g_m}{C_{gs} + C_{sb}}$$
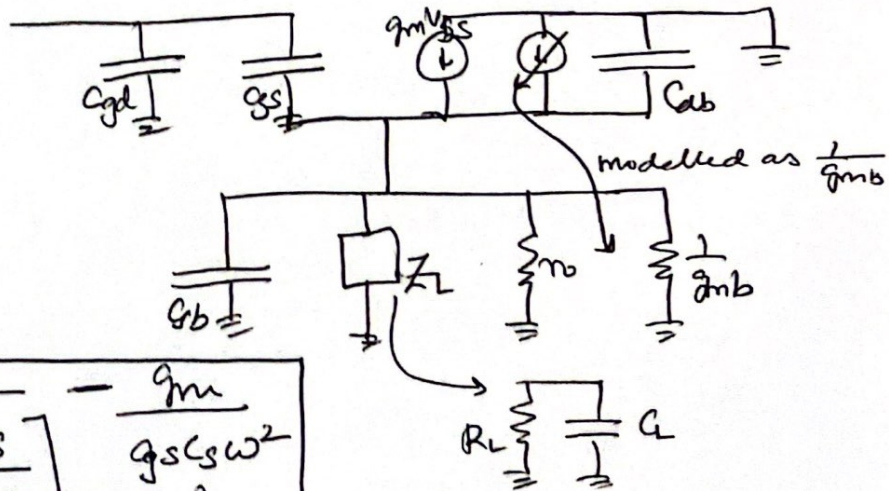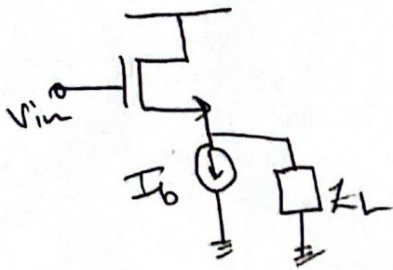
> Rin and Rout have interesting behaviour




$$Z_{in}'(j\omega) = \frac{1}{j\omega \left[\frac{C_{gs} C_s}{C_{gs} + C_s} \right]} - \frac{g_m}{g_s C_s \omega^2}$$

Where $C_s = C_{sb} + C_{load}$.

$$Z_{in} = Z_{in}' \parallel S_{gd}$$

A negative resistor $\Rightarrow$ active element & it can compensate for a lossy circuit. However, it is a short in frequency.


∴ Rout of C.D

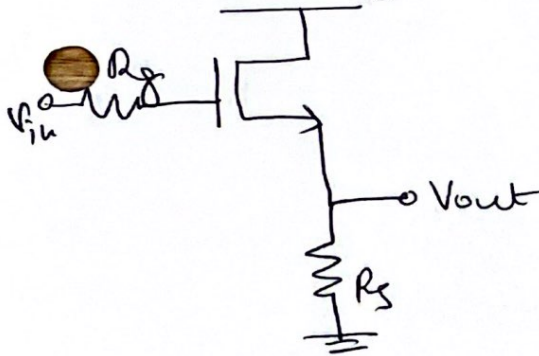

$$Z_{out} = Z_{out}' \parallel Y_o \parallel \frac{1}{g_{mb}} \parallel \frac{1}{sC_{db}}$$

$$Z_{out}' = \frac{R_g (C_{gs} + C_{gd})s + 1}{(R_g C_{gd}s + 1)(sC_{gs} + g_m)}$$

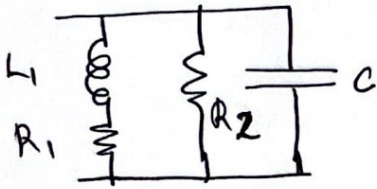Z_{out}' can be modelled as the following RHC circuit



$$C = \frac{C_{gs} C_{gd}}{C_{gs} + C_{gd}}$$



$$R_1 \approx \frac{1}{g_m}$$

$$R_2 = \frac{R_g (C_{gs} + C_{gd})}{C_{gs} \left(\frac{C_{gs}}{C_{gs} + C_{gd}} \right) + g_m R_g C_{gd}}$$

$$L = \frac{R_g (C_{gs} + C_{gd})}{g_m}$$

∴ It has an inductive element in it

Common gate

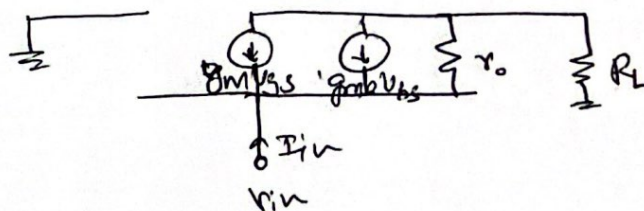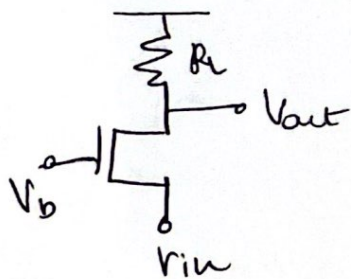

$$R_{in} = \frac{R_L + r_o}{1 + (g_m + g_{mb}) r_o}$$

$$\approx \frac{1}{g_m + g_{mb}} \quad \text{where } r_o \gg R_L$$

↳ Independent of R_L *


$$A_{ro} = \frac{R_L}{R_s + \frac{1}{g_m + g_{mb}}}$$

$$\omega_{p1} = \left[R_s \parallel \frac{1}{g_m + g_{mb}} \right] (C_{gs} + C_{sb})$$

$$\omega_{p2} = \left[R_L (C_{gd} + C_{db}) \right]^{-1}$$

$$A_v = \frac{A_{ro}}{\left(\frac{s}{\omega_{p1}} + 1 \right) \left(\frac{s}{\omega_{p2}} + 1 \right)}$$

Cas code

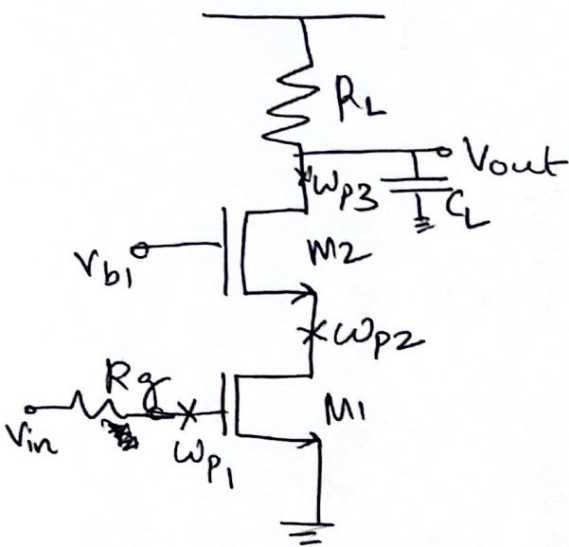

When active load is used
 ω_{p2} remains same since
 ω_{p3} acts as a short when
 we reach frequency of ω_{p2} .

* Usually output pole is dominant

$$\omega_{p1} = \frac{1}{R_g [C_{gd1} (1 + g_{m1} \frac{1}{g_{m2} + g_{mb2}}) + C_{gs1}]}$$


$$\omega_{p1} \approx \frac{1}{R_g [2C_{gd1} + C_{gs1}]} \quad \text{when } M_1, M_2 \text{ are identical}$$

$$\omega_{p2} = \frac{1}{\left[r_{o1} \parallel \frac{1}{g_{m2} + g_{mb2}} \right] \times \left\{ C_{gd1} \left(1 + \frac{g_{m2} + g_{mb2}}{g_{m1}} \right) + C_{db1} + C_{gs2} + C_{sb2} \right\}}$$

$$\text{dominant } \omega_{p3} = \frac{1}{(R_L \parallel \frac{1}{g_{m2}}) \{ C_{gd2} + C_L + \dots \}}$$

Frequency ↔ Time

Amplifier
Single pole

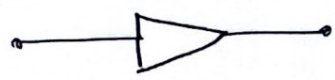


$$A_r = \frac{A_{r0}}{\frac{s}{\omega_p} + 1}$$

Step re

$$V_i(t) = V_a u(t)$$

$$V_o(t) = V_a A_{r0} [u(t)] - V_a A_{r0} [e^{-\omega_p t} u(t)]$$
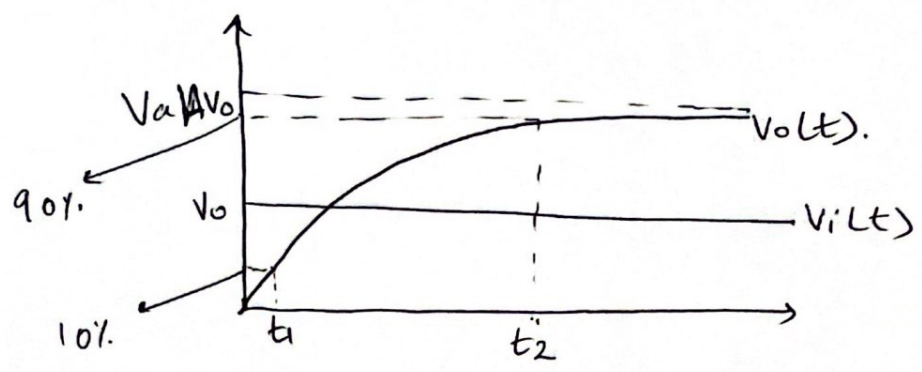
$$V_o(t) = V_a A_{r0} [1 - e^{-\omega_p t}] u(t)$$



$$t_r = t_2 - t_1$$

$$t_r = \frac{2.2}{\omega_{-3dB}}$$

For single pole or dominant pole systems.




$$t_{ref} = \frac{0.7}{f_{H3}} \Rightarrow f_{H3} = \frac{0.7}{t_{ref}}$$

$$f_{H3} \approx 0.7 \text{ data rate}$$

$$t_r = \frac{0.35}{f_{H3}}$$

Cascade of n amplifiers

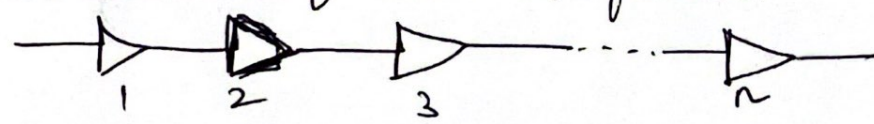

$$A_{r_{tot}} = \left[\frac{A_{r0}}{\frac{s}{\omega_p} + 1} \right]^n$$

$$\omega_{-3dB} = \omega_p \sqrt{2^{1/n} - 1}$$


n = 2 ⇒ $\omega_{-3dB} = 0.64 \omega_p$
 BW drops by 36%
 Gain is squared

$$t_{r_{tot}} = \sqrt{t_{r1}^2 + t_{r2}^2 + \dots + t_{rn}^2}$$

→ when all stages have only one pole

Bandwidth Enhancement

Shunt Peaking

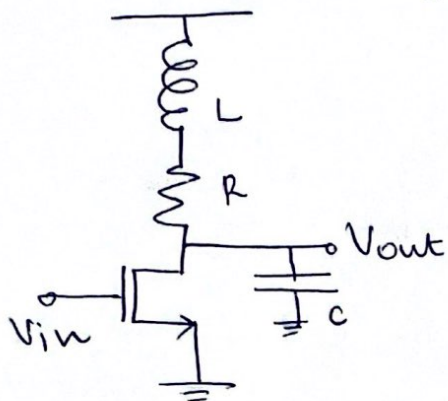

$$Z_L(s) = \frac{R \left[\frac{sL}{R} + 1 \right]}{s^2 LC + sRC + 1}$$

$$|Z_L(j\omega)| = R \sqrt{\frac{(\omega\tau)^2 + 1}{\left(1 - \frac{\omega^2\tau^2}{\omega_1^2}\right)^2 + \left(\frac{\omega}{\omega_1}\right)^2}}$$

where, $\tau = \frac{L}{R}$

$\omega_1 = \omega_{3dB}$
without L

$\omega_1 = \frac{1}{RC}$


Scenario (i)

Maximum Bandwidth $\Rightarrow \frac{\partial Z_L}{\partial \tau} = 0$ & find τ

Substitute τ in $|Z_L|$ & $= \frac{1}{\sqrt{2}} \cdot R$
 $L \rightarrow Z_L(0)$

We get, $\tau = \frac{1}{\sqrt{2}\omega_1}$ & $BW = 1.85\omega_1$
85% higher

However we get Shunt Peaking.

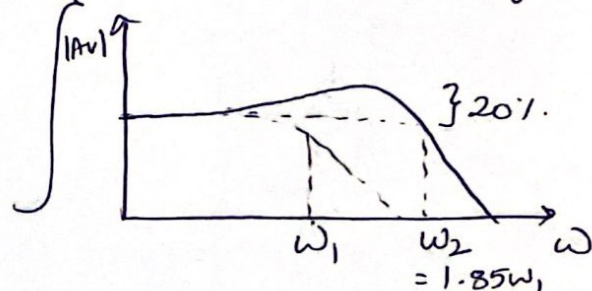

Scenario (ii)

We force peaking to happen after ω_1

$\Rightarrow |Z_L(j\omega)|_{\omega=\omega_1} = R$ we get $\tau = \frac{1}{2\omega_1}$ & $BW \approx 1.8\omega_1$

Scenario (iii)

No peaking $\Rightarrow \frac{\partial Z_L}{\partial \tau}$ does not change sign. $\Rightarrow \tau = \frac{1}{(1+\sqrt{2})\omega_1}$ & $BW = 1.72\omega_1$

The cost of doing this is the phase response!
(Check notes on)

Scenario (iv)

Need to make sure t_g vs. ω is flat } $\Rightarrow \frac{dt_g}{d\omega}$ does not change sign.


$$\Rightarrow \boxed{T = \frac{1}{3.1\omega_1}} \quad \& \quad \boxed{BW = 1.6\omega_1}$$

II Adding a zero to the Transfer Function


$$A_r = A_{r0} \cdot \frac{(1 + \frac{s}{\omega_z})}{(1 + \frac{s}{\omega_p})}$$

However if there is design mismatch $\Rightarrow$ $T_z = \alpha T_p$

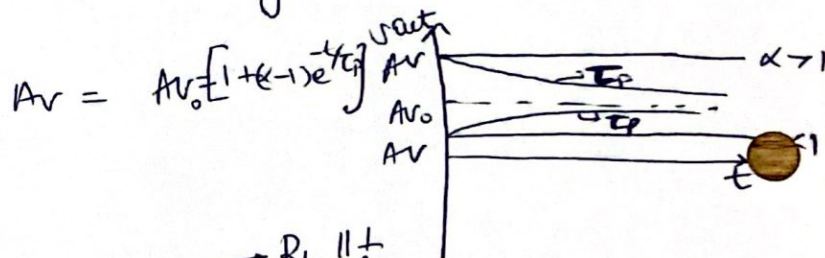The bandwidth may increase but settling time will also increase.



How can we implement it?


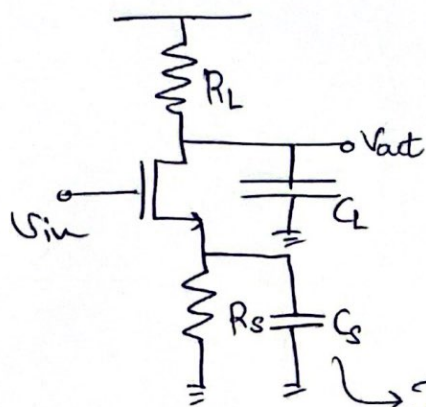


$$A_r = - \frac{Z_L}{\left[\frac{1}{sC_S} \parallel R_S \right] + \frac{1}{g_m}}$$

$$\text{If } R_S \gg \frac{1}{g_m} \Rightarrow \boxed{A_r = - \frac{Z_L}{Z_S}}$$

This gives a '0' But in reality it also gives a pole!

Phase Response

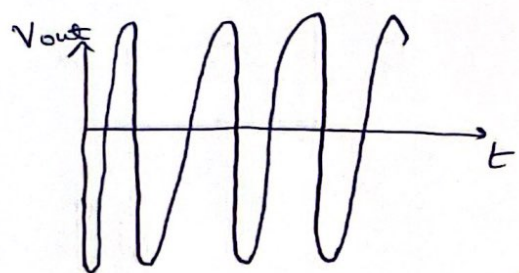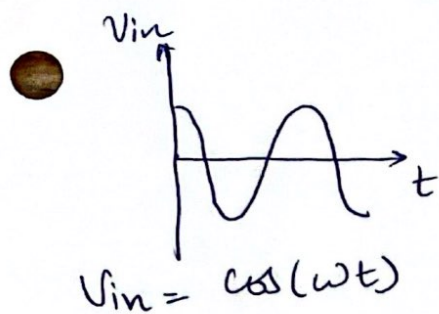

$$= A \cos(\omega(t - t_d))$$

Phase Delay

Here

$$t_d = -\frac{\phi}{\omega}$$

Amount of delay in signal introduced by the system.

2 tone signal



$$V_{out}(t) = 2|A| \underbrace{\cos\left(\frac{\omega_1 - \omega_2}{2}t + \left(\frac{\phi_1 - \phi_2}{2}\right)\right)}_{\text{Envelope}} \underbrace{\cos\left(\frac{\omega_1 + \omega_2}{2}t + \left(\frac{\phi_1 + \phi_2}{2}\right)\right)}_{\text{Information } (\omega_1 - \omega_2)}$$

Group delay

$$t_g = -\frac{(\phi_2 - \phi_1)}{\omega_2 - \omega_1}$$

Envelope

∴ Envelope carries the information we care about.



•

for multitone signals.

$$t_g = -\frac{d\phi}{d\omega}$$


Slope of ϕ over ω .
(Bode plot).

Bode plot

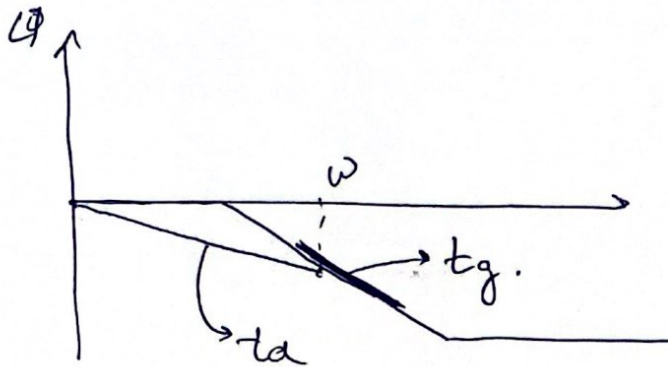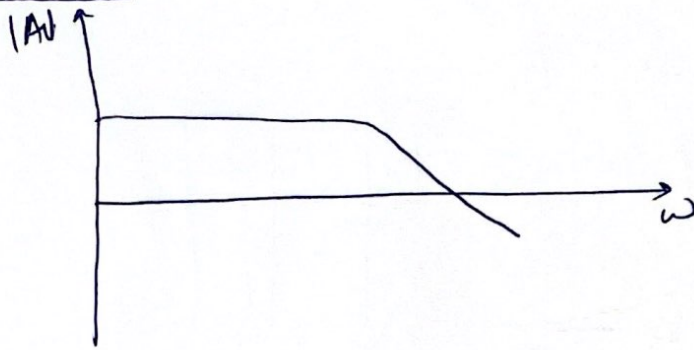

At some ω , the group delay is slope of line.
 * phase delay is $\frac{\phi(\omega)}{\omega}$

→ In pursuit of higher and higher bandwidth in $|A_v|$ vs ω we should not ignore how phase response changes. Ideally we want $t_d = t_g$ at all ω . However they should at least be the same sign.

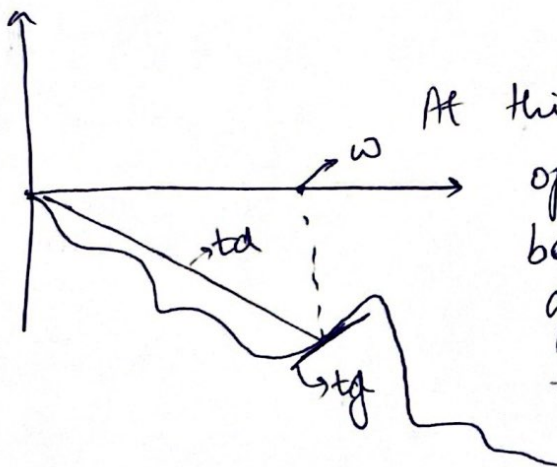




At this frequency the t_d & t_g have opposite sign. → Each signal has been shifted forward but the group has shifted backward in time.

∴ Differential Pair

> Immune to noise.

> Double the swing.
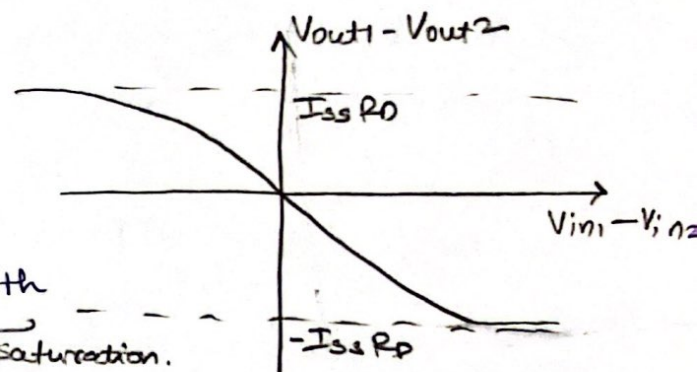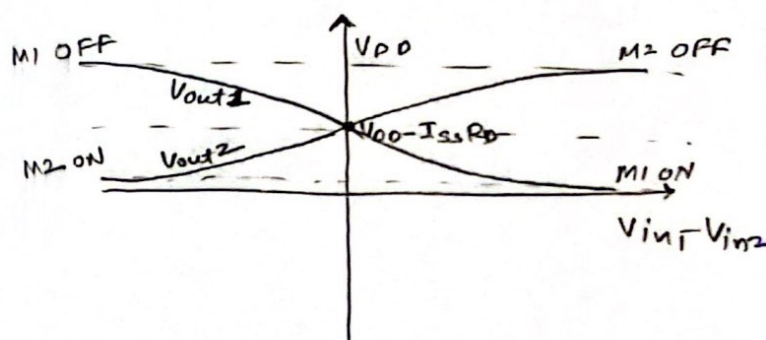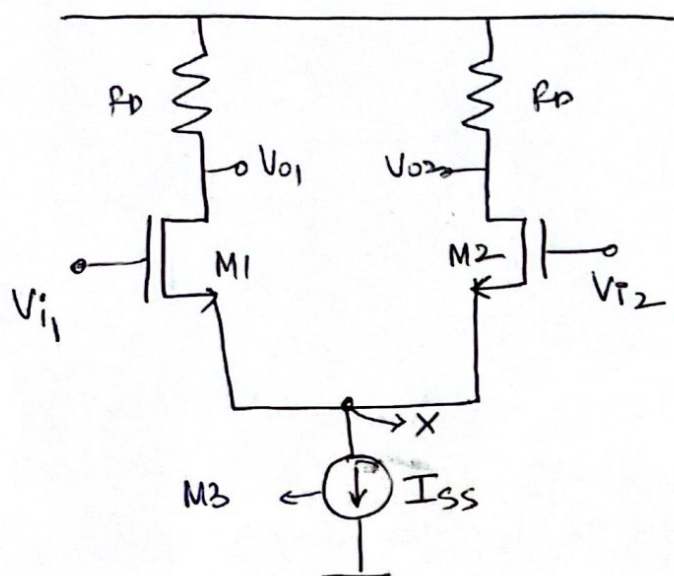
> Output/gain not a strong function of input. ∴ more constant & stable gain.



Range of V_{CM} common mode bias

$$\rightarrow \underbrace{V_{GS1,2} + V_{DS3}}_{\text{to keep } M_1, M_2 \text{ ON}} < V_{CM} < \underbrace{V_{DD} - \frac{I_{SS} R_D}{2} + V_{th}}_{\text{To stay in saturation.}}$$

$$\star I_1 - I_2 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[V_{id} \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - V_{id}^2} \right]$$



$$\rightarrow I_{1,2} = \frac{I_{SS}}{2} \pm \frac{1}{4} \mu_n C_{ox} \frac{W}{L} \left[V_{id} \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - V_{id}^2} \right]$$

$$\rightarrow G_m = \frac{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2 V_{id}^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - V_{id}^2}}$$

$$\rightarrow V_{id, \max} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

To keep both transistors ON

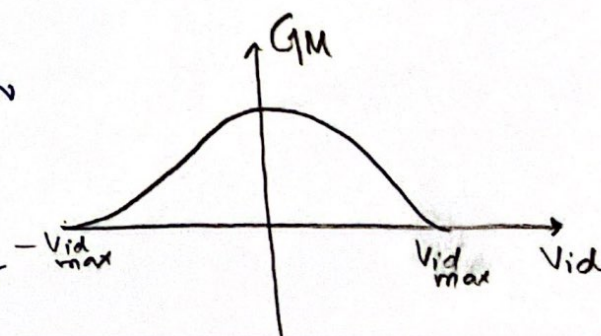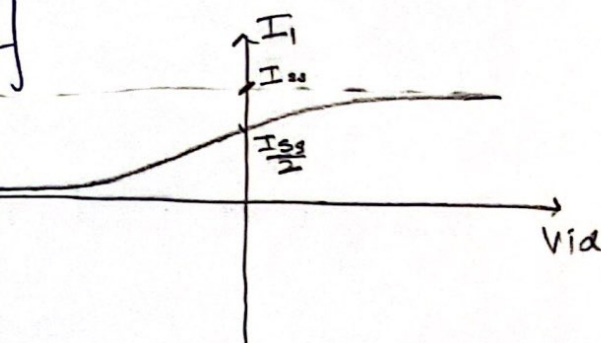→ Note:- When V_{CM} is differential 'X' is a virtual ground & the circuit can be split into two identical circuits to be analysed.




Observations

① $\frac{W}{L} \uparrow \Rightarrow V_{id, \max} \downarrow$

gain $\uparrow$ but swing at $\downarrow$

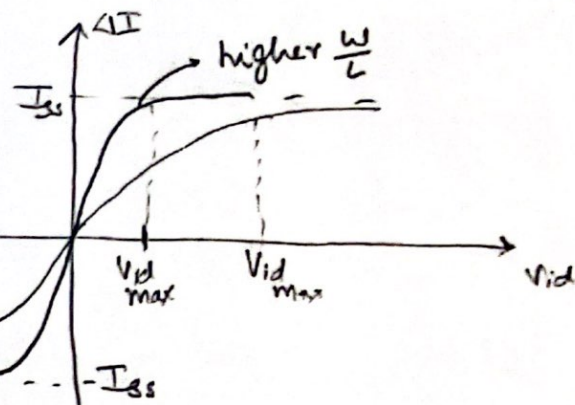
$\Rightarrow$ All current flows through one transistor faster because it is bigger.



② $I_{ss} \uparrow \Rightarrow V_{id, \max} \uparrow$

gain is same, swing at $\uparrow$

$\rightarrow$ Higher power consumption

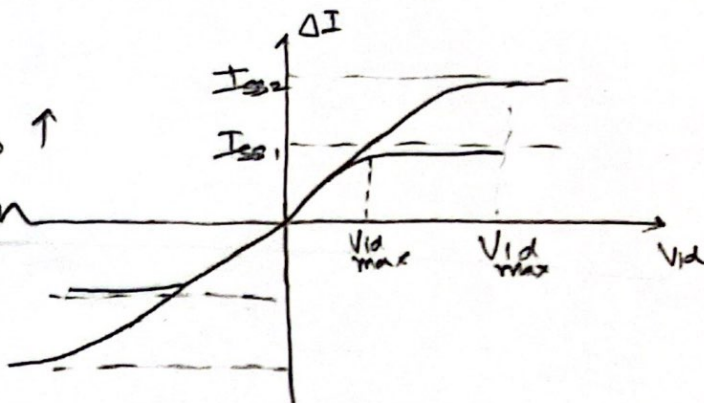

$\rightarrow$ When V_{in} changes by small amount, all the change appears across the V_{gs} and V_x acts as a virtual ground. This is the beauty of this topology. Remember this is only for differential inputs and small signals.

$\rightarrow$ $A_{vd} = -g_m (R_{out})$

Same gain as single side?
Not really since current consumption is double. If power is constant gain $\downarrow$ by $\sqrt{2}$.

$\rightarrow$ CM input DM output $\Rightarrow A_{v_{cm, dm}} = 0$
 $\rightarrow$ DM input CM output $\Rightarrow A_{v_{dm, cm}} = 0$ } Ideally.

$\rightarrow$ CM input CM output $\Rightarrow A_{v_{cm, cm}} = \frac{-R_D}{\frac{1}{g_m} + 2R_{SS}}$

$\rightarrow$ Ideally should be 0 since $R_{SS} \rightarrow \infty$ and we don't have a virtual ground.

Mismatch

Resistor mismatch

● $R_1 = R, R_2 = R + \Delta R$

$$\Rightarrow A_{v_{cmom}} = \frac{\Delta R_0}{R_0} \cdot A_{v_{cmcm}}$$

→ In case of threshold mismatch g_m changes.

→ Common mode rejection ratio CMRR

$$CMRR = \frac{A_{v_{dmom}}}{A_{v_{cmom}}}$$

How well can the circuit reject common signals like noise.
Ideally $\rightarrow \infty$.

$$SNR = \frac{(A_{v_{dmom}} \cdot V_{in_{dm}})^2}{(A_{v_{cmom}} \cdot V_{in_{cm}})^2}$$

g_m mismatch


$$g_{m1} = g_m; g_{m2} = g_m + \Delta g_m$$

$$A_{v_{cmom}} \approx \left| \frac{\Delta g_m}{g_m} \right| \cdot A_{v_{cmcm}}$$

Δg_m is small.

● Active load Differential Amplifier $\Rightarrow$ Single ended output
Higher gain

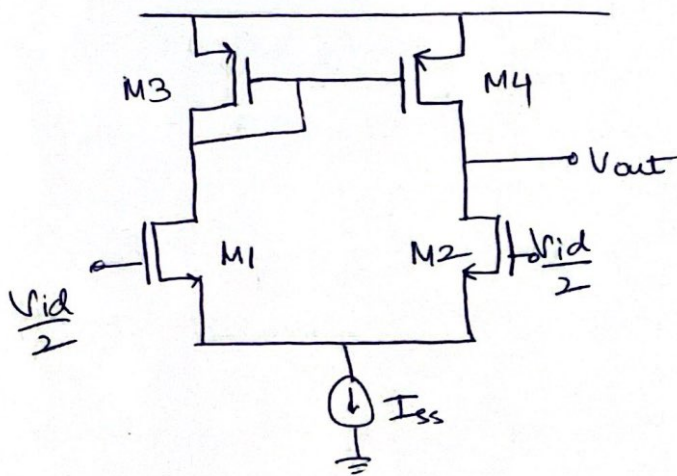→ Very difficult to bias 3 current sources. So we copy current from one line to another and only bias I_{SS} .



$$G_m = g_{m1}$$

$$R_{out} = r_{o2} \parallel r_{o4}$$


$$A_{v_{dm}} = g_{m1} (r_{o2} \parallel r_{o4})$$

$$A_{v_{cm}} = \frac{\frac{1}{2g_{m3,4}} \parallel \frac{r_{o3,4}}{2}}{R_{SS} + \frac{1}{2g_{m1,2}}}$$

$$A_{v_{cm}} \approx \frac{1}{2g_m R_{SS}} \rightarrow \text{Not so good.}$$

so far so good

Frequency Response of Diff. Amp

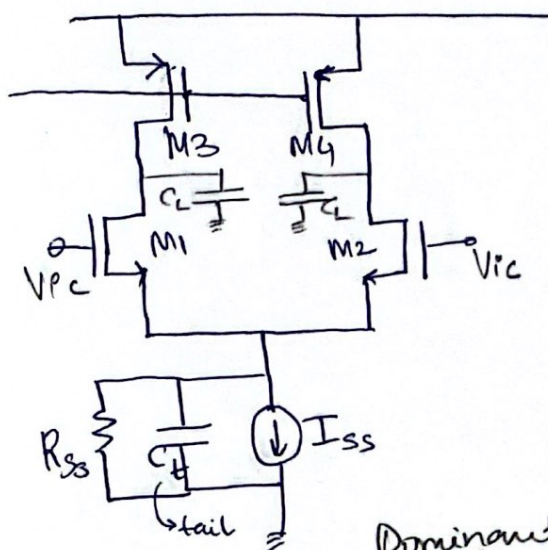

Assuming we could bias it

$$A_{v,CM,DM} = \frac{\Delta g_m \cdot R_D (R_{SS} C_{TS} + 1)}{(R_D C_{LS} + 1) (R_{SS} (g_{m1} + g_{m2}) + 1 + R_{SS} C_{TS})}$$

$$\omega_z = \frac{1}{R_{SS} C_t}$$

Dominant Pole
"Let's ignore it"


$$\omega_{p1} = \frac{1}{R_D C_L}$$

$$\omega_{p2} \approx \frac{g_{m1} + g_{m2}}{C_t}$$

$$R_D = r_{o1} || r_{o3}$$


$$R_{SS} = R_{SS}$$

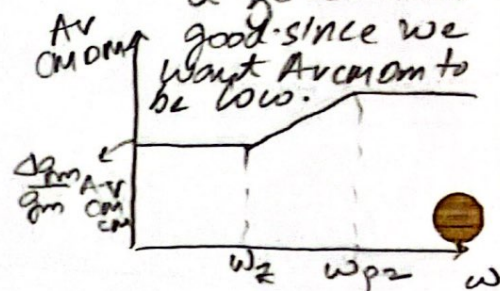tail capacitor has added a pole and a zero. Not good since we want $A_{v,CM,DM}$ to be low.



→ The tail cap causes significant problems when we look at $A_{v,CM,DM}$.

Active load

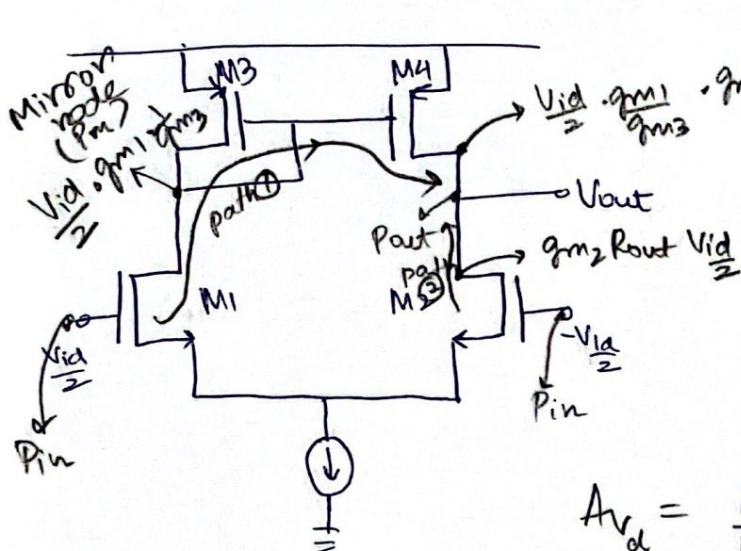

$$P_m = \frac{1}{g_{m3} (2 C_{gd1} + C_{db1} + C_{db3} + C_{gs3} + C_{gs4} + C_{gd4})}$$



since miller effect & gain of M1 is -1

No miller effect since output pole is at low freq. & gain is 0 when we reach P_m

$$D(s) = \left(\frac{s}{P_{in}} + 1 \right) \left(\frac{s}{P_{out}} + 1 \right)$$


$$A_{v,d} = \frac{A_{v,d0}}{D(s)} = \left[\frac{\frac{s}{2P_m} + 1}{\frac{s}{P_m} + 1} \right]$$

Effect of P_m

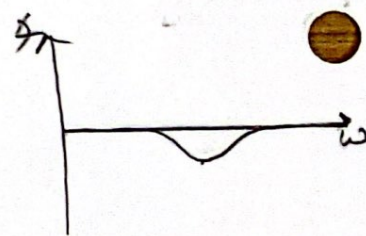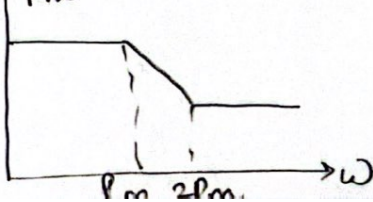

→ $P_m \approx 2P_m$ are less than a decade apart so there is a small dip in phase response, which is annoying.

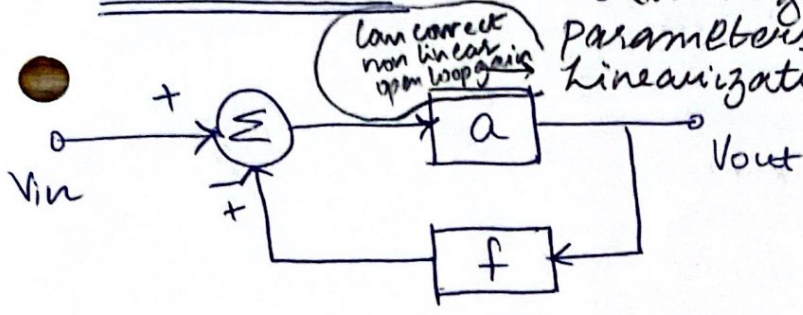Feedback → Higher bandwidth.
 → Desensitizing the gain w.r.t transistor parameters. as long as gain is high.
 Linearization!



$$\frac{V_{out}}{V_{in}} = \frac{a}{1+af}$$



Loop gain (T)

$$A = \frac{a}{1+af}$$

→ Relative variation in ~~loop~~ open loop gain has a small effect on total gain $\left\{ \frac{dA}{A} = \frac{da}{a} \left(\frac{1}{1+af} \right) \right\}$

→ Variation in feedback gain has a larger effect so we try to keep feedback as a passive element $\left\{ \frac{dA}{A} = \frac{df}{f} \left(-\frac{af}{1+af} \right) \right\}$

Frequency Response

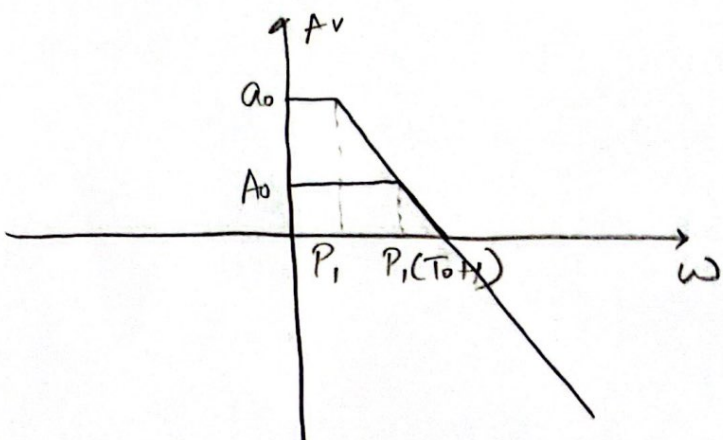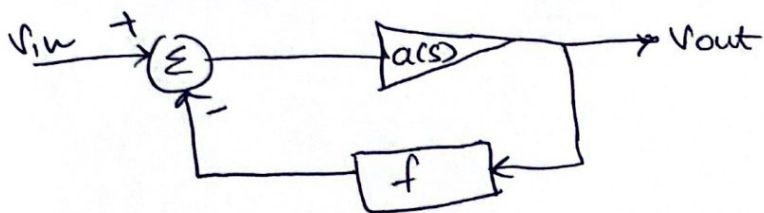

Ideal case of only one pole.

$$A(s) = \frac{A_0}{\frac{s}{P_1(Tot)} + 1}$$

$$A_0 = \frac{a_0}{a_0f + 1}$$


$$a(s) = \frac{a_0}{\frac{s}{P_1} + 1}$$

→ Adding feedback can compromise gain for B.W.

$$A_0 \rightarrow \frac{a_0}{1+T}$$



$$BW \rightarrow BW(1+T)$$

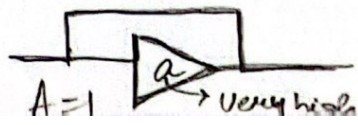⇒ Ideal buffer trades all the gain for B.W




→ As $af \rightarrow \infty$, pole $\rightarrow -\infty$ & gain $\rightarrow 0$

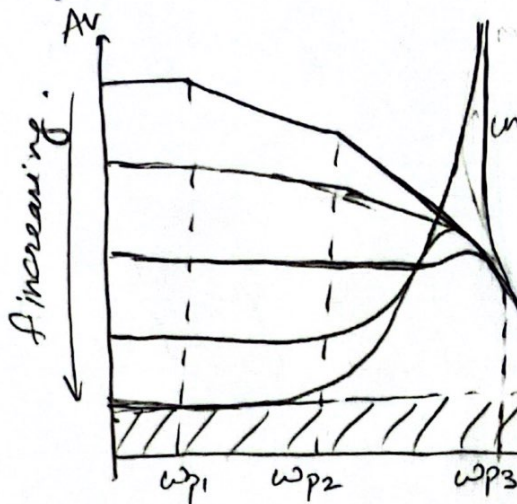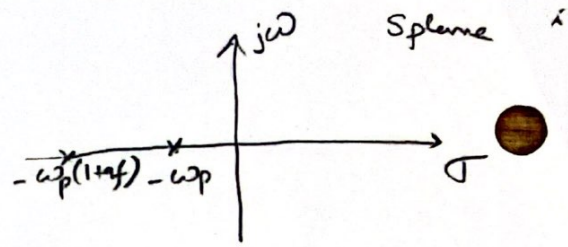→ However in reality we have more than one pole and as $f \uparrow$ we start seeing shooting in the gain and system becomes unstable.



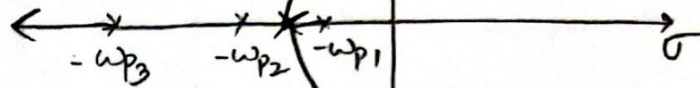
As f increases $\omega_{p3} \rightarrow -\infty$ & ω_{p1} & ω_{p2} and move to the side of $j\omega$ but each hit the $j\omega$ axis = unstable.



When we have complex poles we start seeing ringing.

→ As we further increase f the peaking might go down but the time domain response actually goes to ∞ .

Stability

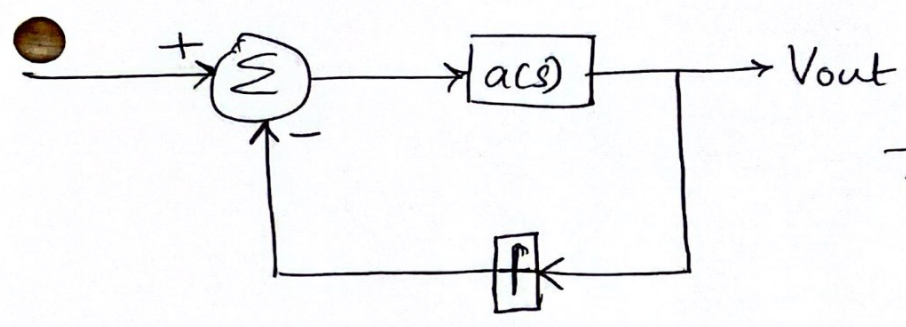

$T = af \rightarrow$ loop gain
 $A = \frac{a}{1+af}$

Marginally stable

$|af| = 1$
 $\angle af = \pm 180^\circ$

therefore we want to avoid
 $|af| > 1$ & $\angle af = -180^\circ$
 $\downarrow$ $\downarrow$
 $0dB$ -180°


Unstable

$|af| > 1$
 $\angle af = -180^\circ$

Stable


$|af| < 1$
 $\angle af = \pm 180^\circ$

on s plane :-

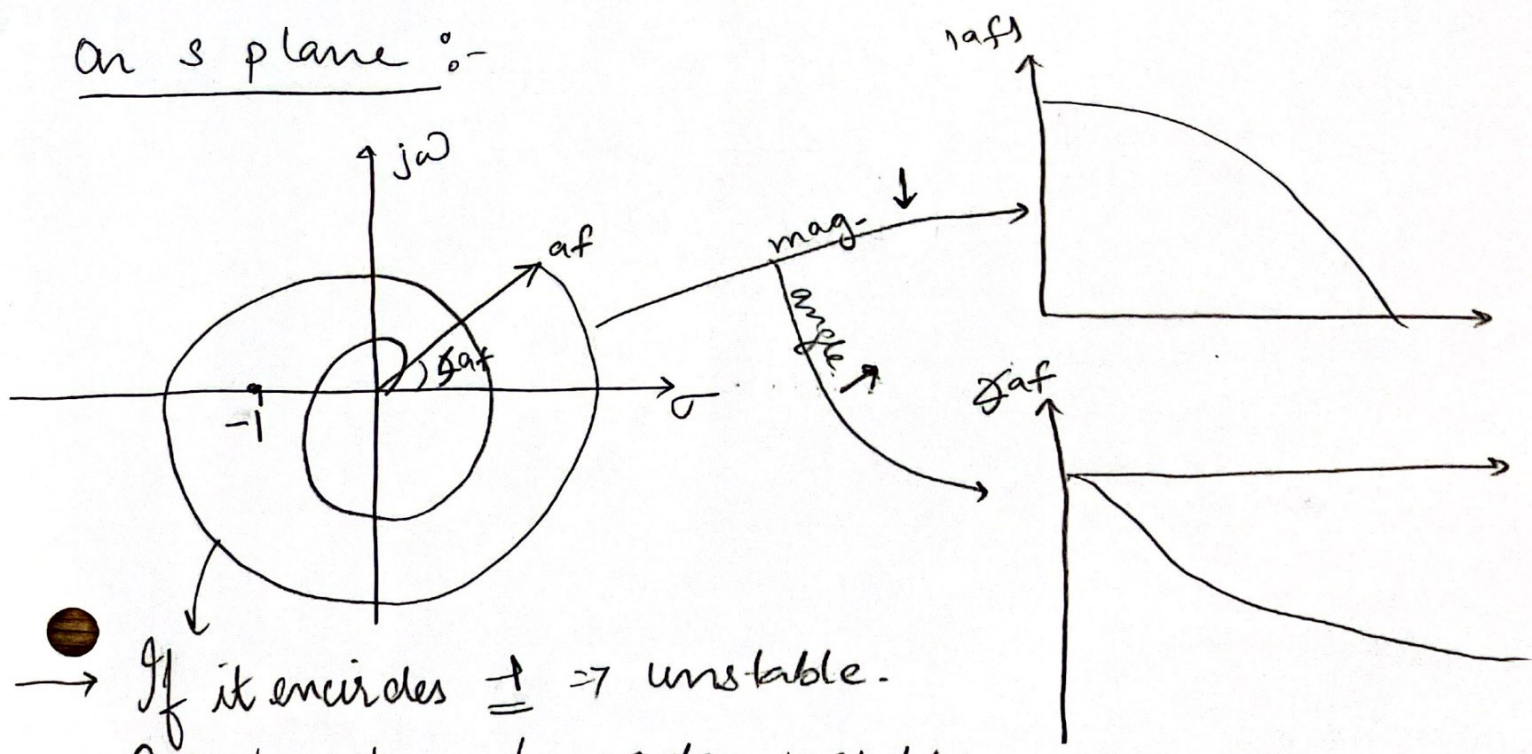

- If it encircles $\pm 1 \Rightarrow$ unstable.
- Only true if open loop system is stable.

Gain and Phase Margins

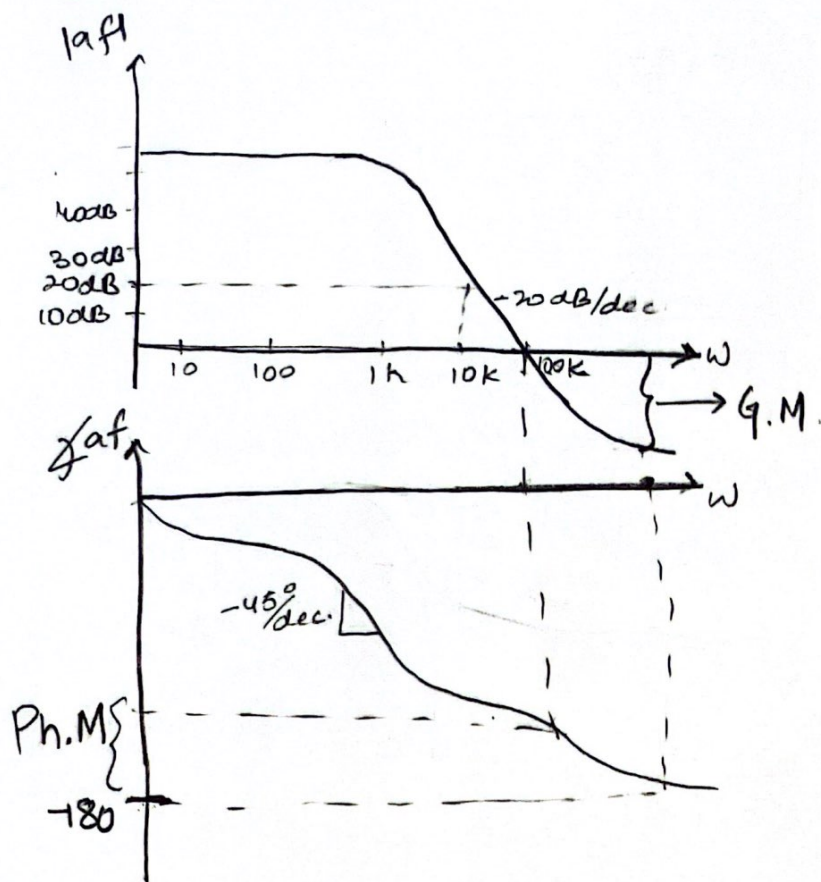

Gain Margin

At $\angle af = -180^\circ$ how much room is left before hitting the dreadful 0dB.

$$G.M = \frac{1}{|af| \text{ at } \omega_{180^\circ}}$$

Phase margin

At $|af| = 1$ how much phase is left before hitting the dreadful -180° .

$$Ph.M = 180^\circ + \angle af \text{ at } \omega_{0dB}$$


→ For a system $A(s) = \frac{A_0}{\left(\frac{s}{\omega_{p1}} + 1\right)\left(\frac{s}{\omega_{p2}} + 1\right)\left(\frac{s}{\omega_{p3}} + 1\right)}$

$$|A(j\omega)| = 20 \log \frac{\omega}{\omega_{p1}} + 20 \log \frac{\omega}{\omega_{p2}} + 20 \log \frac{\omega}{\omega_{p3}}$$

$$\angle A(j\omega) = -\tan^{-1} \frac{\omega}{\omega_{p1}} - \tan^{-1} \frac{\omega}{\omega_{p2}} - \tan^{-1} \frac{\omega}{\omega_{p3}}$$


When poles are at least 1 decade apart. Not sure otherwise.

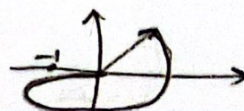→ GM & Ph.M may be high but small change in PVT could make the system unstable. Need to look at s-plane to get the full picture.



→ if it turns a little it becomes unstable

→ In our 3 pole system

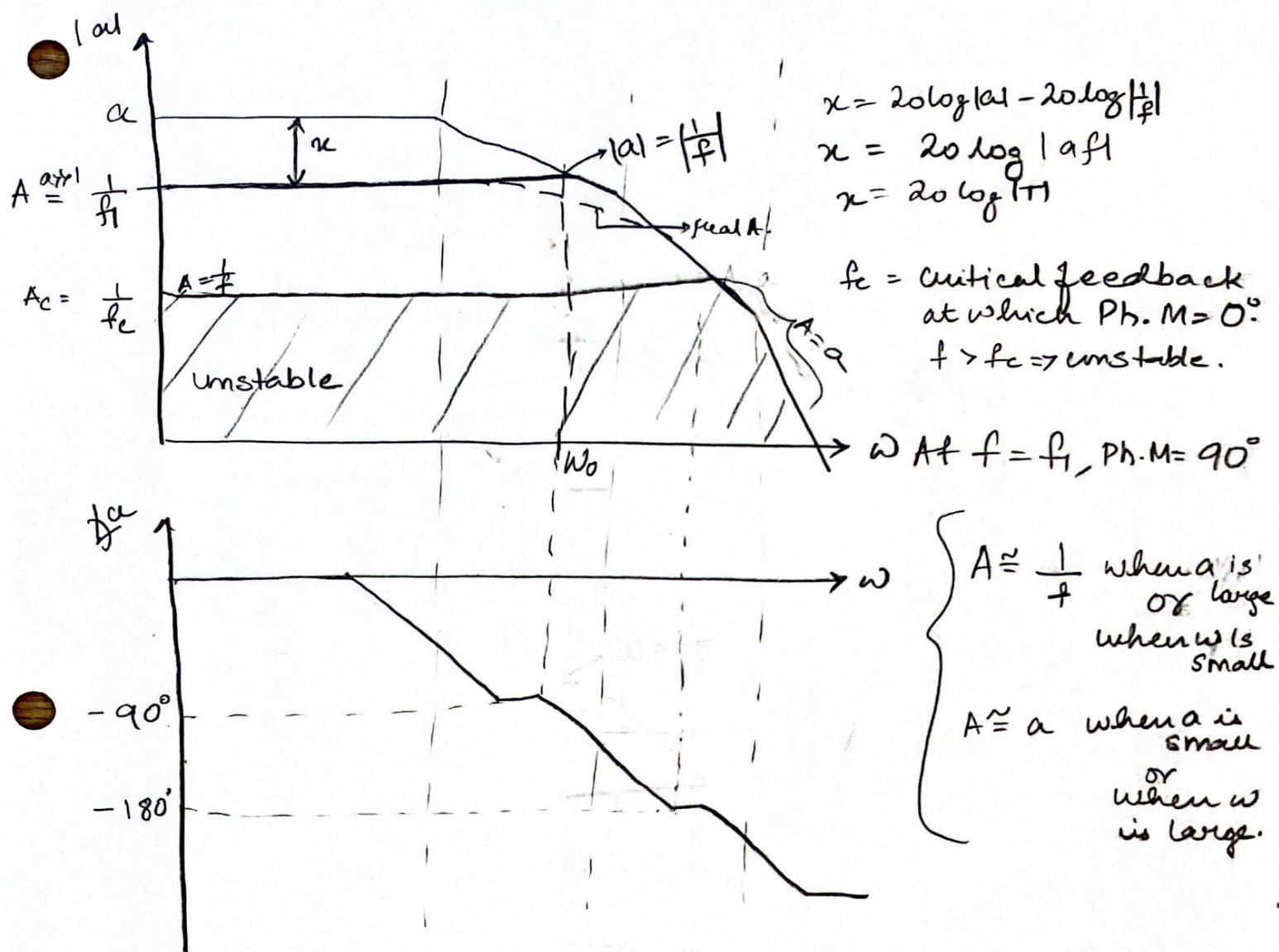

At ω_0 :- $|af|=1$ and $|A| = \frac{|a|}{|1+a(j\omega)f|}$

Assume Ph. M at $\omega_0 = 90^\circ$


$$|A| = \frac{|a| \omega_0}{|1 + a(j\omega_0)f|}$$

$$\angle a(j\omega)f = -90^\circ$$

$$|a(j\omega_0)f| = 1$$

$\Rightarrow |A| = \frac{|a|}{\sqrt{2}} \Rightarrow \text{magnitude of } A < a \text{ which is expected}$
 $\Rightarrow \text{it is 3dB lower.}$



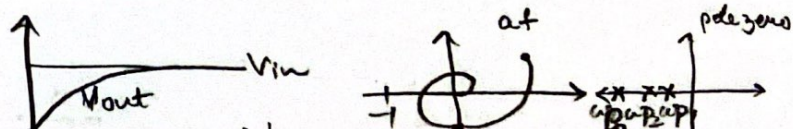
$\Rightarrow$ System is well behaved $\Rightarrow$



→ Ph. M = 60°

$$\Rightarrow |A|_{\omega_{at}} = \frac{|a|}{|1 + 1e^{-j(120^\circ)}|} = \underline{\underline{|a|}}$$

→ There is 3dB peaking so that $|A|$ and $|a|$ are same.

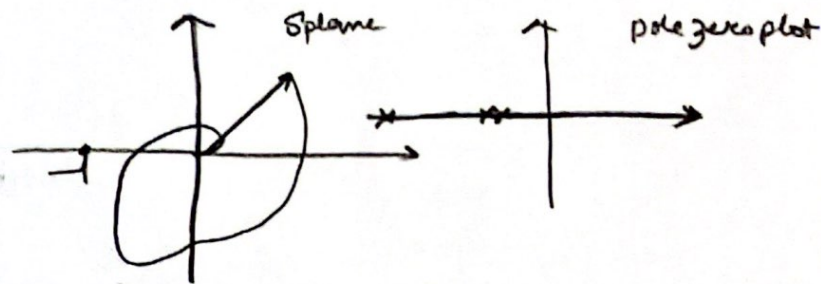
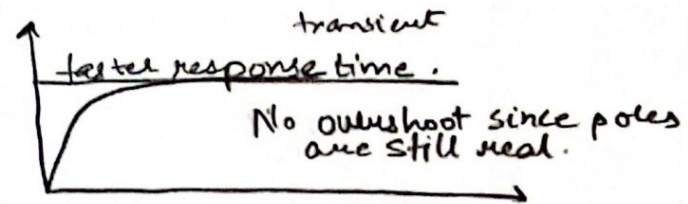
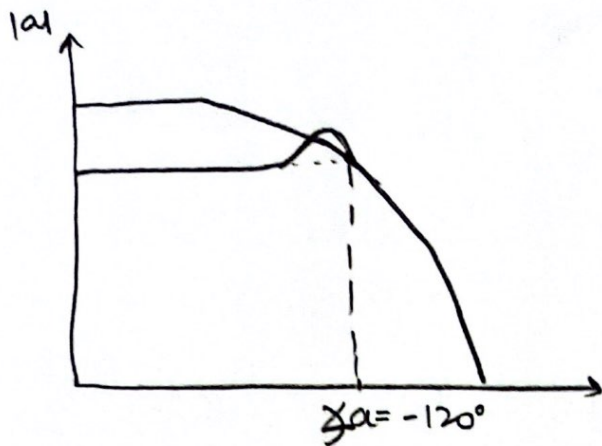


→ Ph. M = 45° → popular case.

$$\angle a = -135^\circ$$





$$|A| = \frac{|a|}{|1 + 1 \cdot e^{-j(135^\circ)}|}$$

$$|A| = 1.3 |a|$$


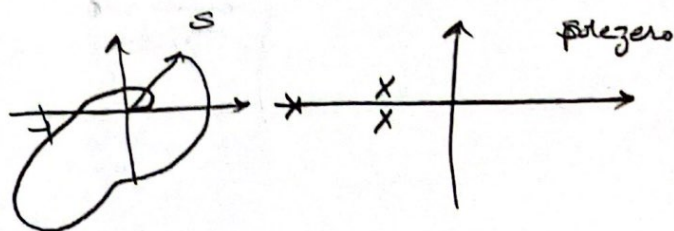
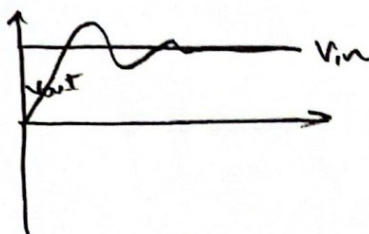
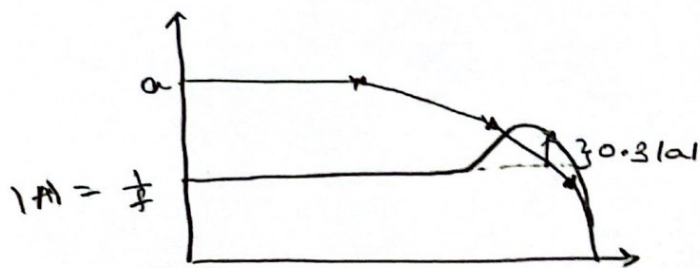


Phase margin = 30° $\angle a = -150^\circ$

$|A| = 5|a|$

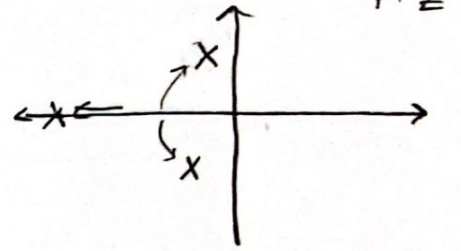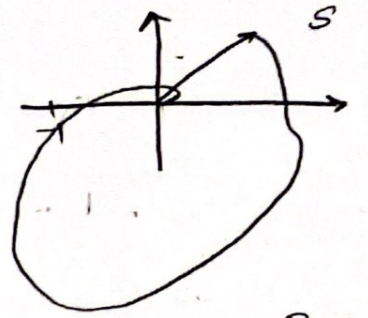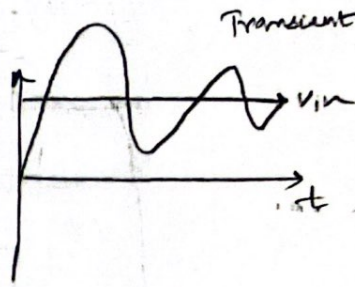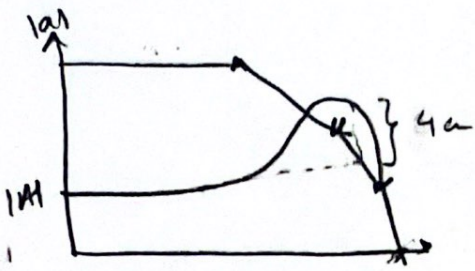

Phase Margin = 0°

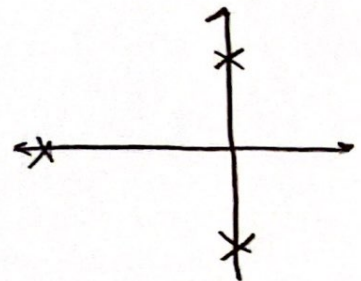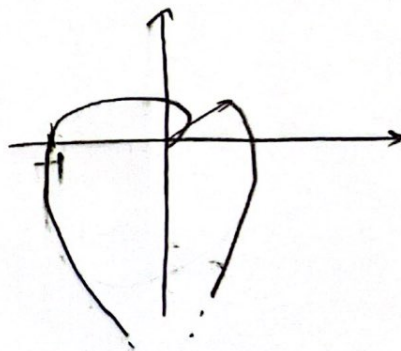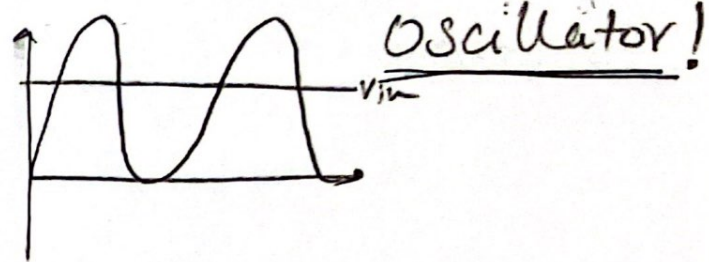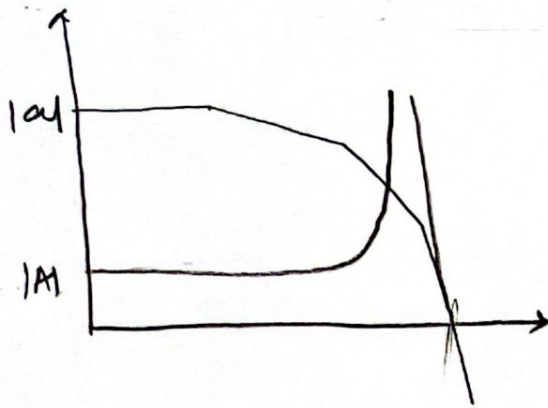


→ We need to change 'a' so that even at max feedback $f=1$ we do not lose stability. Solution:- Give up the BW.

Frequency Compensation.

→ Let's say we want $\text{Ph.M} = 45^\circ$ when $f=1$.
 $\Rightarrow \left. \begin{array}{l} |a|_{\omega_0} = 1 \\ \angle a|_{\omega_0} = -135^\circ \end{array} \right\}$

Method ① Decrease |phase| to meet -135° when $|a|=1$
 → Better since B.W is not lost. However much harder to implement.

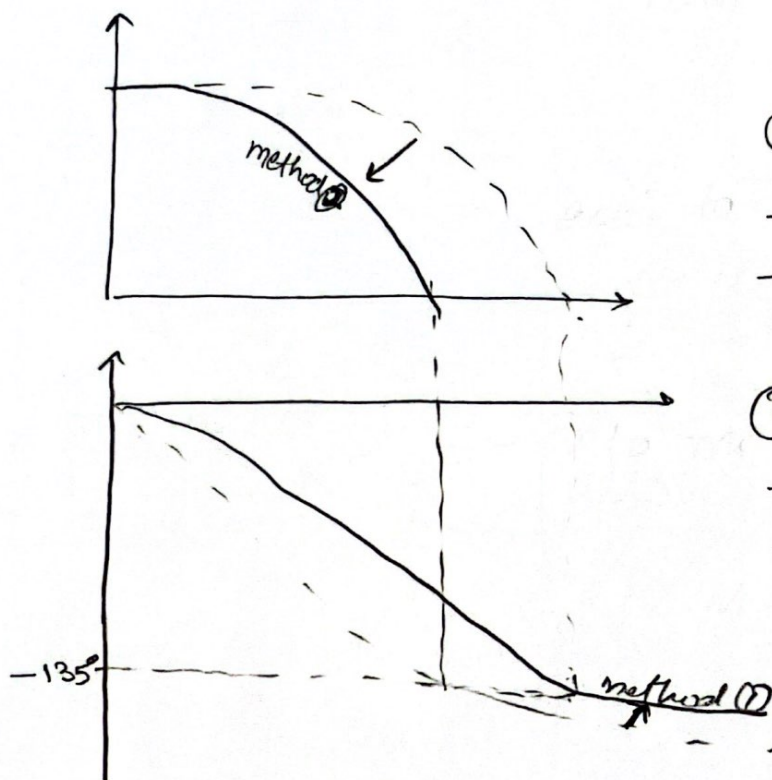Method ② Decrease gain to meet 1 when $\angle a = -135^\circ$.
 → Easier to implement.



Influence of Zeros

- ① Left half plane zero.
 → Increase both $|a|$ & $\angle a$.
 → May or may not work since we need $|a| \downarrow$ & $\angle a \uparrow$
- ② Right half plane zero.
 → Increase $|a|$ & decrease $\angle a$
 → Really bad since we want $\downarrow |a|$ & $\uparrow \angle a$.


→ How to implement? Add an RC stage that has a low frequency pole.

Steps to add P_{new} :-

- ① Find ω_0 where current poles give -45° since new pole should give $-90^\circ \Rightarrow \text{total} = -135^\circ$
- ② From ω_0 in $|a|$ trace back @ -20 dB/dec & see where it hits $|a| \Rightarrow \omega_{\text{new}}$.
- ③ Add a pole at ω_{new} & redraw $|a|$ & $\angle a$.

Another (Better) Implementation

lower P_1 such that at $\omega_{1/|A| \neq 1}$ we hit $\angle A = -135^\circ$.

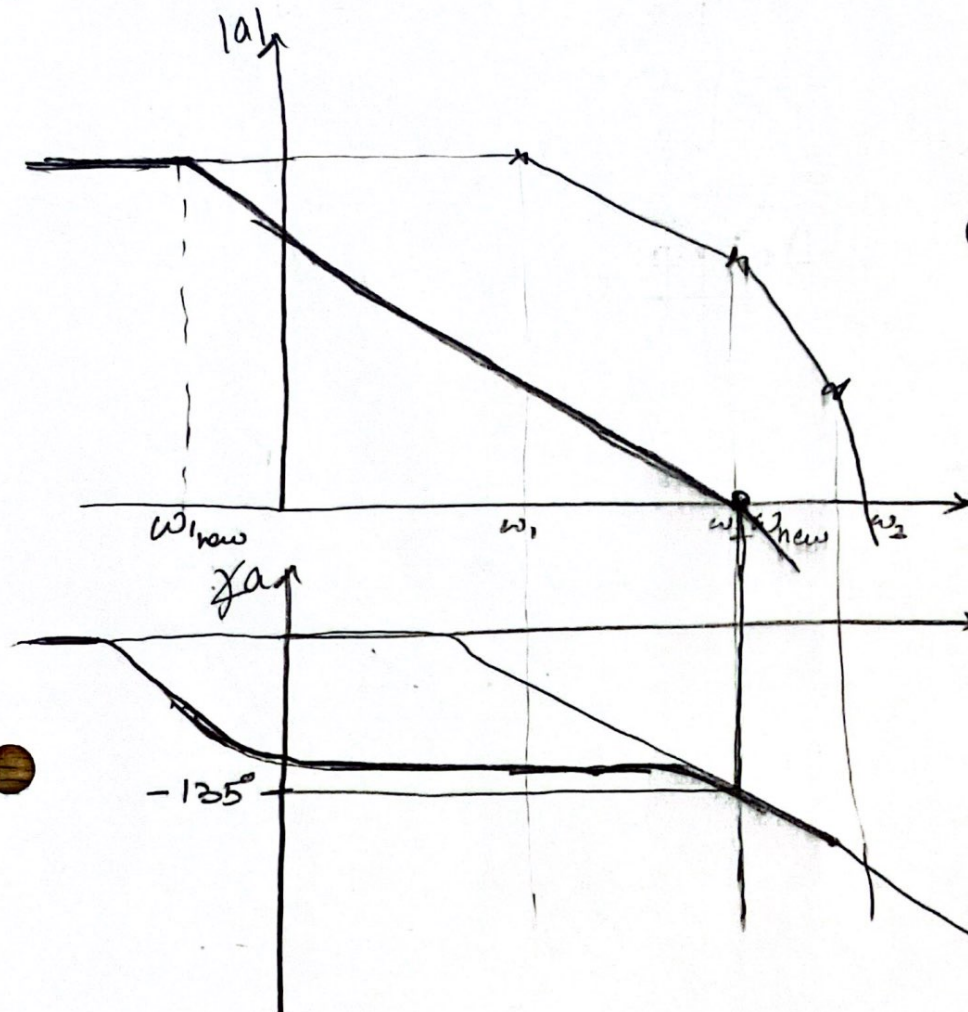


Steps:-

- ① Find ω_0 at which $P_2, P_3 \dots$ give -45° .
- ② From this ω_0 we move up at -20 dB/dec until we hit $|A| = 1$ @ ω_{new} .
- ③ ω_{new} is the new pole frequency of ω_1 .
- ④ Redraw $|A| \times \angle A$.

→ Here ω_2 is the 2dB BW of $|A| \times$ unity BW of $|A|$.

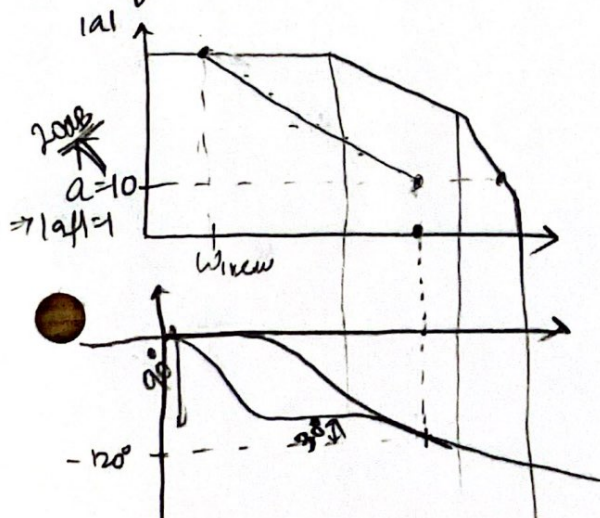→ If $f = 0.1 \times \text{Ph.M} = 60^\circ$.



Steps:-


- ① Find ω_0 at which $P_2, P_3 \dots$ give -30° .
- ② From this freq. we move from $|A| = 10$ to $|A| = 1$. Whenever it hit $|A| = 1$ is our new ω_{new} .

If poles are atleast 1 decade apart:-

$$\angle A(s) = -\tan^{-1} \frac{\omega}{\omega_{p1}} - \tan^{-1} \frac{\omega}{\omega_{p2}}$$

$$|A(s)| = 20 \log \frac{\omega}{\omega_{p1}} + 20 \log \frac{\omega}{\omega_{p2}}$$

Circuit implementation. : opamp example.

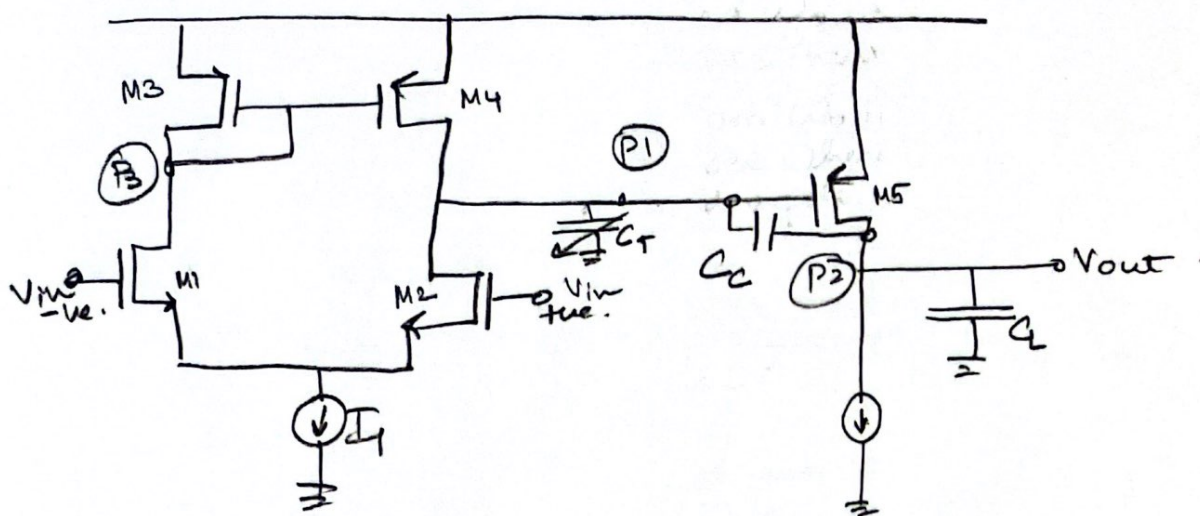

$P1: \frac{1}{R1C1}$ Where $R1 = r_{o2} \parallel r_{o4}$;
 $C1 = C_{gd2} + C_{db2} + C_{gd4} + C_{db4} + C_{gd5}(1 + g_{m5}r_{o5}) + C_{gs5}$

→ no miller since high gain

$P2: \frac{1}{R2C2}$ where $R2 = r_{o5}$
 $C2 = C_L + C_{gd5} + C_{db5}$

→ high gain ⇒ no miller.

P3:- High ⇒ Don't care.

We want to $\uparrow P1 \Rightarrow \uparrow C1 \Rightarrow$ add a capacitor C_T

→ Assuming $P1 \xrightarrow{\frac{1}{R1C1}}$ was 10KHz & we now want it at 1.1Hz.

C_T needs to be 10K times larger than $C1 \Rightarrow$ not realistic to be on chip.



→ But observe miller effect at $C_{gd5} \Rightarrow$ why not increase that by adding a compensation cap there?

→ Notice this C_L should increase $C2$ or lower $P2 \Rightarrow \downarrow BW$ of A

→ In reality it actually moves $P2$ to higher frequencies

→ This is called pole splitting.

Pole Splitting. :- Why does it happen?

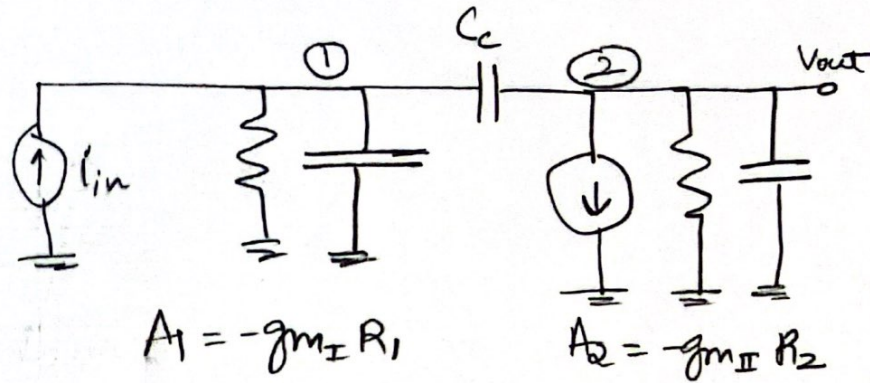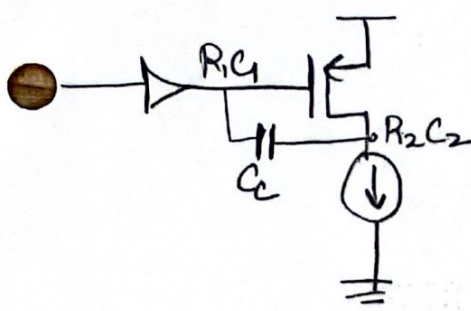

$$\frac{V_{out}}{I_{in}} = \frac{R_1 R_2 [C_c s - g_{m5}]}{1 + s [R_1 (C_c + C_1) + R_2 (C_c + C_2) + R_1 R_2 g_{m5} C_c] + R_1 R_2 s^2 [C_c C_1 + C_c C_2 + C_1 C_2]}$$

notice $S_z = \frac{g_{m5}}{C_c} \rightarrow$ right half plane zero $\rightarrow$ very bad!
will deal with it later.

Assuming dominant pole :-

$$P_1 = \frac{1}{R_1 (C_c + C_1) + R_2 (C_c + C_2) + R_1 R_2 g_{m5} C_c}$$

If $C_c \gg C_1, C_2 \times g_{m5} R_1 R_2 \gg R_1, R_2$

$$P_1 = \frac{1}{R_1 R_2 g_{m5} C_c}$$

C_c is boosted by gain of 2nd stage.

What happened to P_2 ?

Assuming dominant pole :-

$$P_2 = \frac{g_{m5} C_c}{C_c (C_1 + C_2) + C_1 C_2}$$

$$P_2 \approx \frac{g_{m5}}{C_1 + C_2} \quad \text{if } C_c \gg C_1, C_2$$

Earlier it was $\frac{1}{R_2 C_2}$. It has moved to higher freq. $\Rightarrow$ Great!


W/o C_c :- $P_1 = \frac{1}{R_1 C_1}$; $P_2 = \frac{1}{R_2 C_2}$

w C_c :- $P_1 = \frac{1}{R_1 C_1 (g_{m5} R_2)}$; $P_2 = \frac{g_{m5}}{C_1 + C_2}$

Becomes much higher
Since: $R_2 \gg \frac{1}{g_{m5}}$


$\Rightarrow$ we regain some lost B.W

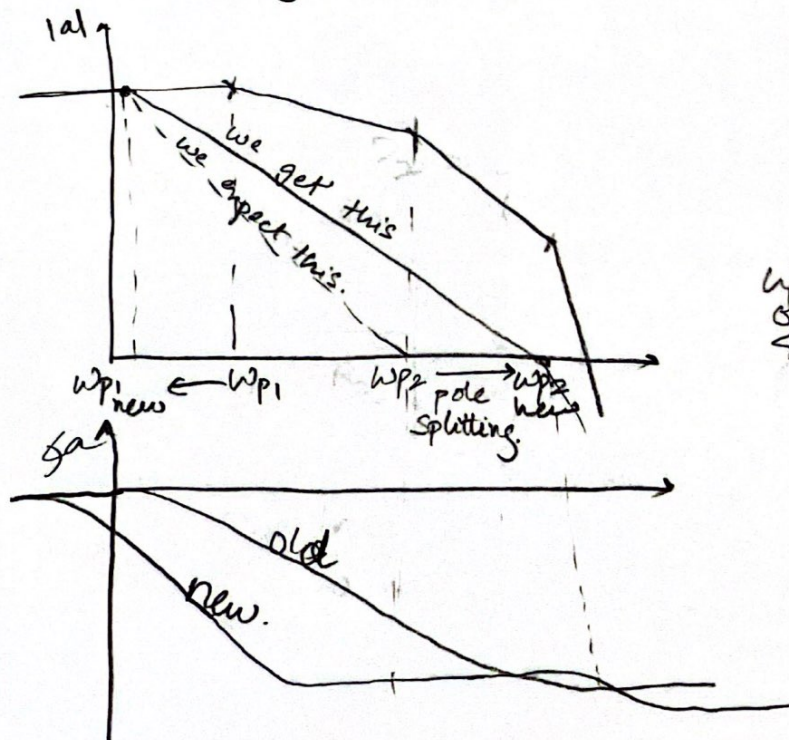(However not all is well since now we have a R.H.P zero). [This is the zero that pushes P_2 to higher frequencies]



$$\omega_{-20dB} \text{ of } A = \omega_{p2_new}$$

Generalizing

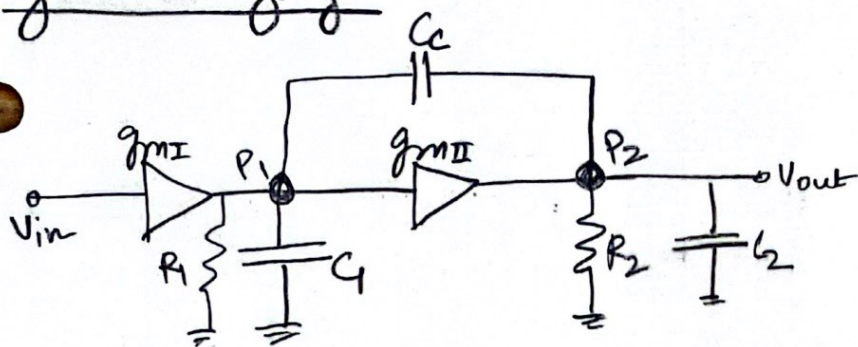

$$P_1 = \frac{1}{R_1(R_2 g_{mII}) C_c}$$

$$Z = \frac{g_{mII}}{C_c}$$

$$P_2 = \frac{g_{mII} C_c}{C_c(C_1 + C_2)}$$

→ System behaves as a single pole system with P_1 as dominant pole.

⇒ GBW product is constant.


$$A = \frac{a}{1 + af} \quad \text{where } a \approx \frac{a_0}{1 + \frac{s}{P_1}}$$

→ gain of $a = a_0$; BW of $a = P_1$

→ gain of $A \approx 1$; BW of $A = a_0 P_1$ if $f \gg 1$ since $GBW = \text{constant}$


Ex:- If $|a| = 10^5$ & $P_1 = 1 \text{ kHz}$.

After $f \gg 1$ $|A| = 1$ & $BW = 10^8 = 100 \text{ MHz}$.

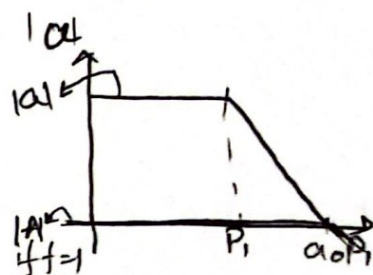

$$\text{If } V_{in} = V_0 \cdot u(t) \text{ (step)} \Rightarrow V_{in}(s) = \frac{V_0}{s}$$

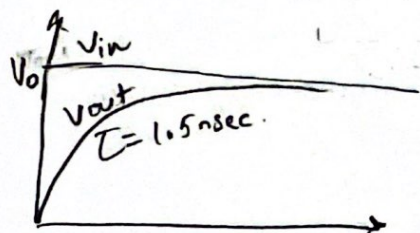O/p would be exponential with $T = \frac{1}{2\pi RC} \approx 1.5 \text{ nsec}$. where $RC = 10^3 \text{ M}$




However this is only true when V_0 is small.

For a large V_0 we see a linear rise in V_{out} . But why?

Answer:- Does not behave like a single pole system anymore. $\Rightarrow$ Slower Rate.

SLEW RATE

Opamp example.

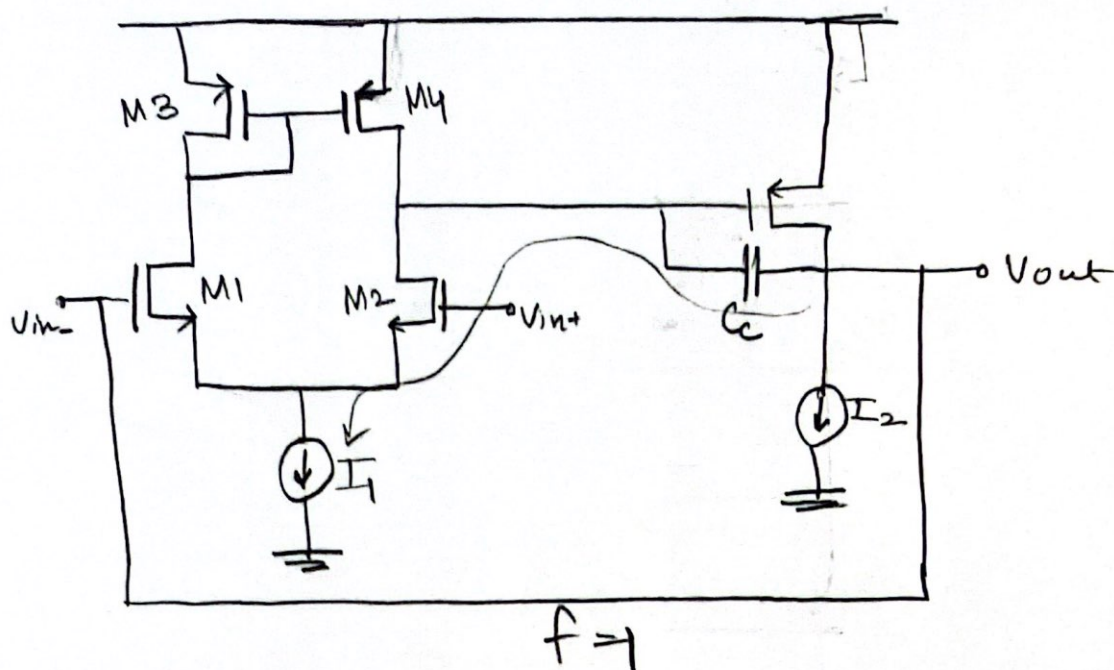


> Initially $V_{in}^+ = V_{out} = V_{in}^- = 0$

> Let's apply $V_{in}^+ = V_{DD}$ (largest V_p) :- at $t=0^+$: M2 ON
M1, M3, M4 {OFF}

> Max V_{in} for it to be differential is $\approx V_{DD}$ but here we applied much larger V_p . $\Rightarrow$ M1 would be completely off since M2 pulls all I_1 .
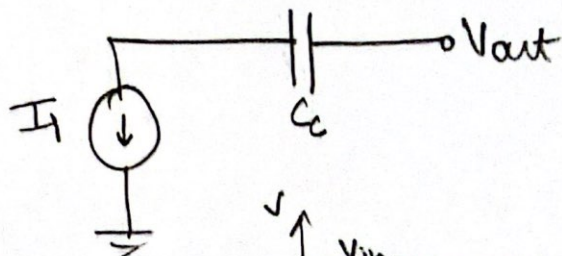
> Now we have a Cap in series with a current source.




$$\Rightarrow I_1 = C_c \cdot \frac{dV}{dt}$$

$$\Rightarrow \frac{dV_{out}}{dt} = \frac{I_1}{C_c} \quad \left. \vphantom{\frac{dV_{out}}{dt}} \right\} \text{Slew rate!}$$

$$\Rightarrow V_{out} = \frac{I_1}{C_c} \cdot t \Rightarrow \text{linear increment.}$$

Slope of this line is Slew rate

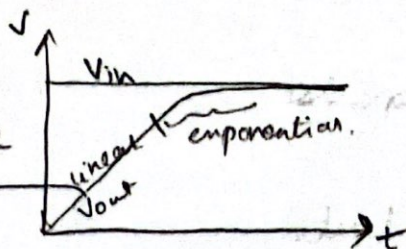

$\rightarrow$ This linear rise continues until $V_{in}^- \uparrow$ due to feedback & $M_{id} < I_1$ - $\Rightarrow$ diff amp starts working, then it's exponential.


$$\rightarrow \therefore \text{Slew Rate} = \frac{I_1}{C_c}$$

• B.W may show τ but S.R. is the real deal because that's how the system actually responds.


$\rightarrow$ This is bad so we need to increase the slewrate.

$\rightarrow$ How? Increase I_1 ? It doesn't work much.

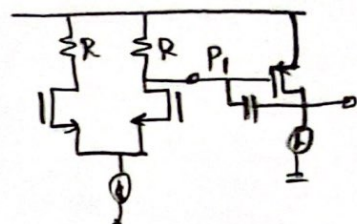$\rightarrow$ To increase $I_1 \Rightarrow R \downarrow \Rightarrow P_i \uparrow$ but we can't change P_i since we designed it. To keep P_i constant we must $C_c \uparrow \Rightarrow SR \downarrow$.



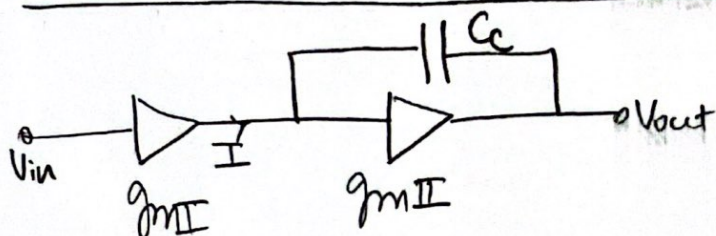
$\rightarrow$ Let's take a closer look at S.R.



$$\frac{\Delta I}{\Delta V_{in}} = g_{mI}$$

$$\frac{\Delta V_{out}}{\Delta I} = R_{out} \approx \frac{1}{g_{mII}} \quad \text{if gain of II is large.}$$
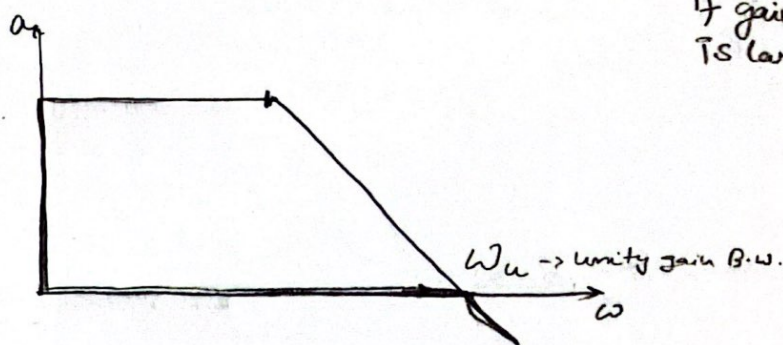
$$\Rightarrow \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{g_{mI}}{g_{mII}}$$



At ω_u :-

$$\left| \frac{\Delta V_{out}}{\Delta V_{in}} \right| = 1$$


$$\Rightarrow \left| \frac{g_{mI}}{g_{mII}} \right| = 1 \Rightarrow \left| \frac{g_{mI}}{j\omega_u C_c} \right| = 1 \Rightarrow \boxed{C_c = \frac{g_{mI}}{\omega_u}}$$

→ $C_c = \frac{g_{mI}}{\omega_u}$ → Not very precise since we are assuming Ph.M is constant. But it gives insight.

→ $S \cdot R = \frac{I_1}{C_c} = \frac{I_1}{g_{mI}} \cdot \omega_u$
 $\Delta V_{out} / \Delta t$

① We could increase B.W:- But this needs to be done during original design and not during frequency compensation.

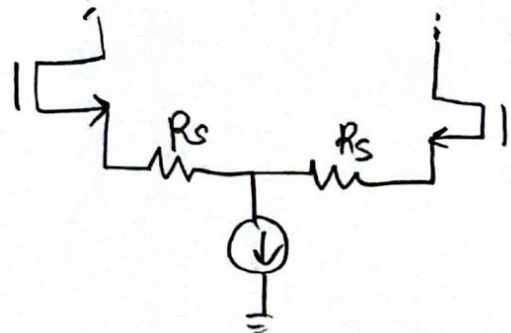
② For a fixed I_1 , need to lower $g_{mI} \Rightarrow$ Degeneration!



$\Rightarrow g_m = \frac{g_m}{1 + g_m R_S} \Rightarrow$ Gain $\downarrow$ } Bad
 Noise $\uparrow$ }
 But SR $\uparrow$ } Good

→ Lesson:- Design such that g_{mI} is very low from the start.

→ Dealing with that annoying RHP zero.

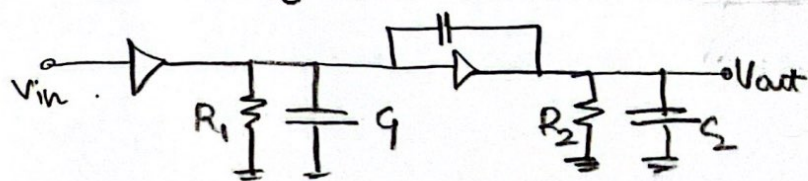


$\begin{cases} z = \frac{g_{mII}}{C_c} \\ p_2 = \frac{g_{mII}}{G + C_2} \text{ if } C_c \gg C_1, C_2. \\ \omega_u = \frac{g_{mI}}{C_c} \end{cases}$

$\frac{z}{\omega_u} \approx \frac{g_{mII}}{g_{mI}} \Rightarrow$ we push z at least one decade after ω_u .
 $\Rightarrow \frac{g_{mII}}{g_{mI}} > 10$

Also notice, $\frac{p_2}{\omega_u} = \frac{g_{mII}}{g_{mI}} \cdot \frac{C_c}{C_1 + C_2} \Rightarrow$ We make $g_{mII} \gg g_{mI}$ so that we can also increase $p_2 \Rightarrow$ W_{bad} of 1st

Another way to fix the RHP zero.

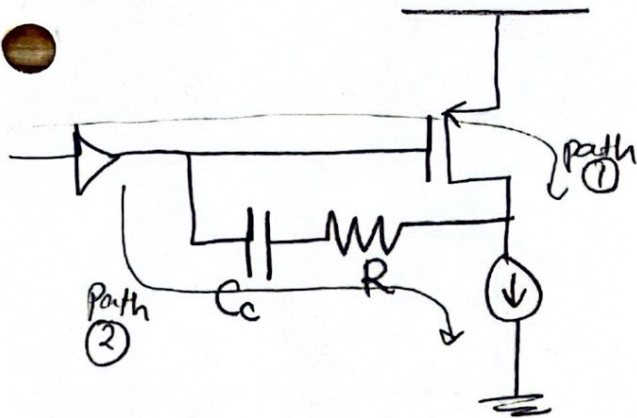


$$z_{w/o R} = \frac{g_{mII}}{C_c}$$

$$z_{with R} = \frac{1}{C_c \left(\frac{1}{g_{mII}} - R \right)}$$

at $R = \frac{1}{g_{mII}}$ z is at $+\infty$

at $R > \frac{1}{g_{mII}}$ z is at $-\infty$

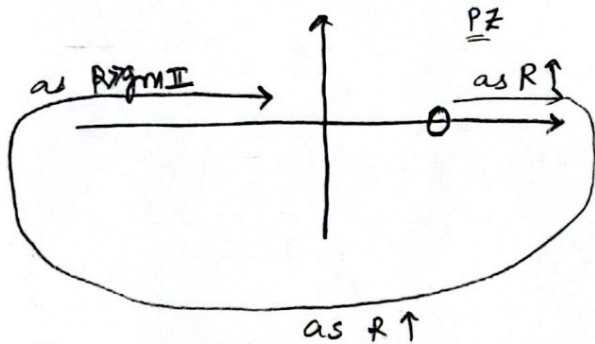at $R \gg \frac{1}{g_{mII}}$ z is in LHP.



→ Intuitively,

Path 1 has 180° phase shift.

Path 2 w/o R has 90° phase shift → adding a zero.

Path 2 w R has $< 90^\circ$ phase shift → reducing the effect of the zero.